 


## Contents


- The synthesis process
- VHDL as a standard for synthesis
- Synthesis aspects and guidelines
- Combinational synthesis
- Sequential synthesis



## Synthesis Process - 1

- Process of turning an abstract, technology independent, text description of a design into gates.
- Two crucial steps:
  - Translation  
acts as the automated bridge between two levels of abstraction
  - Optimization  
technology-specific design transformation to meet user's goals for the given design.

## Synthesis Process - 2

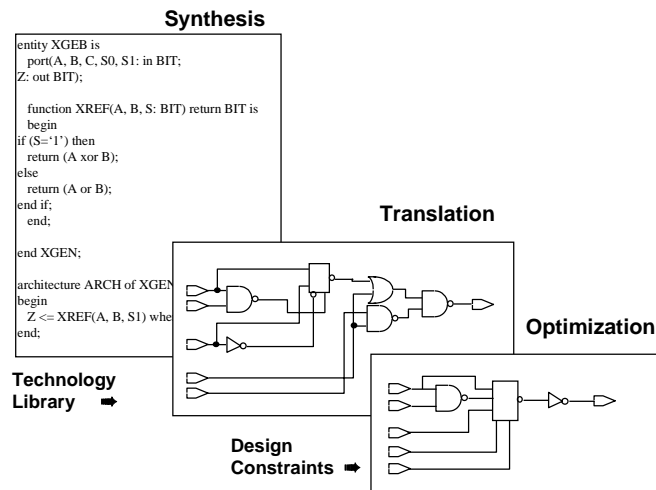


4

## Synthesis Process - 3


- **Translation**
  - In general, from an algorithmic-like description of the behavior to the register transfer level (RTL) to gate level.
- **Optimization**
  - Introduction of user's constraints.
  - Significant aspects: performance, area and test.

5

 

 
## Synthesis Process - 4

- The logic synthesis process begins with a validated behavioral design description.
- The design is translated into a design composed of:
  - control part, and
  - data path
- At the RTL level, the design description has been partitioned down to the implementation primitives of ALUs, ROMs, RAMs, data-path and control functions.



 
## Synthesis Process - 5

- A second component to synthesis design policy in the VHDL style that has been adopted for the specification of the device.
- Different VHDL descriptions of the same functionality can yield radically different results.
- The more the VHDL description yields an implementation (structural description style) the easier the translation phase is; the higher the abstraction level, the more fundamental the translation phase is.



 
## Synthesis Process - 6

- VHDL was aimed at simulation purposes.
  - The semantic is uniquely defined.
    - The same code processed with two different commercial simulators will provide the same results.
    - The simulation task requires no "interpretation" of the code.
  - The semantics of VHDL is expressed in terms of a canonical simulator and not in terms of equivalent hardware constructions.


 
## Synthesis semantics

- VHDL lacks of synthesis semantics.
  - The synthesis task requires an "interpretation" of the code to determine which hardware device can realize the desired function.
- Being synthesis a difficult task, commercial tools usually restrict the set of accepted statements to a tool-dependent subset.
  - No portability
  - No reusability




## Synthesis semantics

- To obtain satisfiable results from the synthesis process, the user has to 'deeply' know the commercial tool.
- A basic idea of what VHDL constructs lead to is also required.
- A "Guide to VHDL synthesized constructs" is useful for selecting the appropriate constructs and having a general feeling of the possible results.

Level-0 VHDL Synthesis Subset


10

 

## Synthesis semantics

- VHDL Synthesis Subset
  - definition of a stable VHDL synthesis usage guide
  - allow portability
  - interchange format between tools, designers, companies ...
  - allow VHDL to be used as an RT/logic specification language
  - facilitate reusability of descriptions


11

 

## Synthesis semantics


- Stable VHDL synthesis usage guide
  - It is important to understand how the tool interprets the VHDL source code
  - It is useful to agree on what the expected results of the synthesis of the VHDL source code should be:
    - less confusion
    - no misunderstanding

12

 


## Synthesis semantics

- VHDL portability

 


- Usually there are several possible styles to describe a behavior:
  - It is advisable to select the statement which is more widely adopted.

13

 

 
## VHDL styles

- Different “styles” describing the same behavior may lead to different realizations.
- An example: Full Adder
  - behavioral
  - data flow
  - structural




14

 

## VHDL styles: behavioral - 1


```
architecture FA_BEH of FULL_ADDER is
begin
  process (X, Y, CIN)
    variable BV: BIT_VECTOR(1 to 3);
    variable NUM: INTEGER range 0 to 3;
    variable STemp, CTemp: BIT;
  begin
    NUM := 0;
    BV := X & Y & CIN;
    for I in 1 to 3 loop
      if (BV(I) = '1') then
        NUM := NUM + 1;
      end if;
    end loop;
  end process;
end architecture;
```

15

 

 
## VHDL styles: behavioral - 2

```
case NUM is
    when 0 => CTemp:='0'; STemp:='0';
    when 1 => CTemp:='0'; STemp:='1';
    when 2 => CTemp:='1'; STemp:='0';
    when 3 => CTemp:='1'; STemp:='1';
end case;
SUM <= STemp ;
COUT <= CTemp ;
end process;
end FA_BEH;
```




## VHDL styles: behavioral - 3

 



## VHDL behavioral - 4

 


## VHDL styles: data flow - 1

```

architecture FA_BOOL of FULL_ADDER is
  signal S1, S2, S3: BIT ;
begin
    S1 <= X xor Y ;
    SUM <= S1 xor CIN after 1 ns;
    S2 <= X and Y ;
    S3 <= S1 and CIN after 1 ns;
    COUT <= S2 or S3 after 1 ns;
end FA_BOOL;
  
```

## VHDL styles: data flow - 2

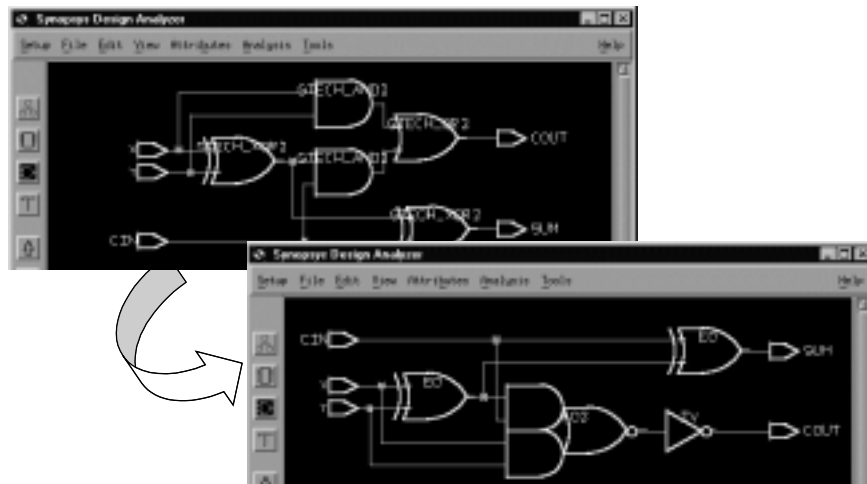

20


## VHDL styles: structural - 1

```


architecture FA_ST of FULL_ADDER is
    component HALF_A
        port(A, B: in BIT;
            S, C: out BIT);
    end component;
    component OR_GATE
        port(A, B: in BIT;
            O: out BIT);
    end component;
    signal C1, S1, C2: BIT;
begin
    HA1: HALF_A port map (A=>X, B=>Y, S=>S1, C=>C1);
    HA2: HALF_A port map (S1, CIN, SUM, C2);
    OR1: OR_GATE port map (C1, C2, COUT);
end FA_ST;

```


21

 

## VHDL styles: structural - 2

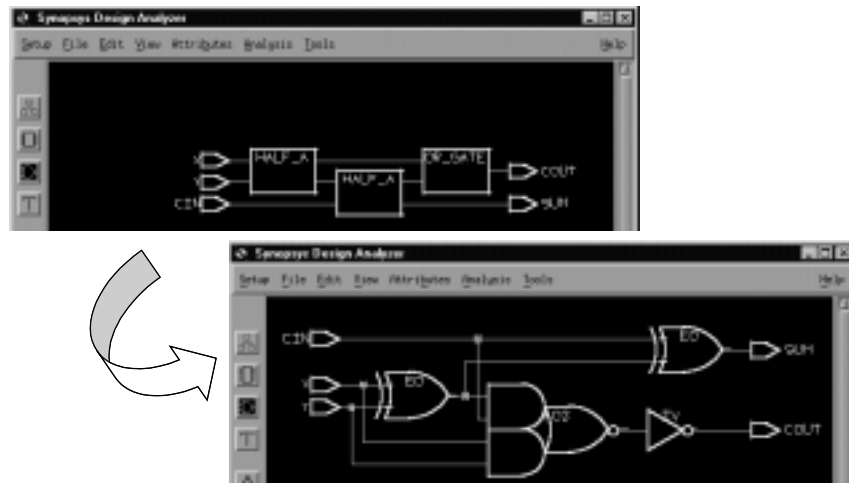


22

 

## Some considerations

- General aspects of some elements in relation with VHDL synthesis:
  - Vectors
  - Arithmetic, Logical & Relation operands
  - Subtypes, slices and functions

23

 


## VHDL: vectors

```
entity ex1 is
  port(A, B, C: in bit_vector(1 to 5);
        Z: out bit_vector(1 to 5));
end ex1;
architecture arch of ex1 is
begin
  process(A,B,C)
    variable TEMP: bit_vector(1 to 5);
  begin
    TEMP := A and B;
    Z <= TEMP xor C;
  end process;
end;
```

Bit-to-bit operations


24

 

## VHDL: Turning Integer into Vectors


- Declare range for INTEGER objects for implementation of the minimum possible bits.
- If a signal (or port) or variable is declared to be of type INTEGER without specifying a range, a tool may implement the object using a full 32 bits.
  - The automatic tool warns the user of an unconstrained signal/variable declaration

25

 


## VHDL: Turning Integer into Vectors - 1

Bolchini · Ferrandi · Fummi

 


26

 


## VHDL: Turning Integer into Vectors - 2

Bolchini · Ferrandi · Fummi

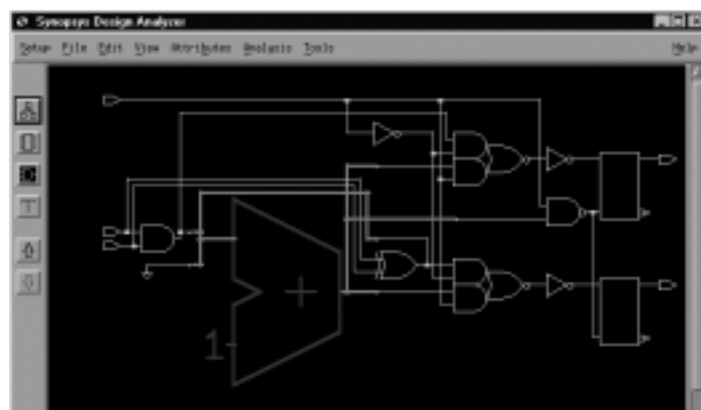



27

 
  
## VHDL: vector indexes - 1

```
entity EX is
  port(A: in BIT_VECTOR(0 to 3);
        OU : out BIT) ;
end EX ;
```

```
architecture EX_1 of EX is
begin
  OU <= A(2) ;
end EX_1 ;
```



## VHDL: vector indexes - 2

```
entity EX_VAR is
  port(A : in BIT_VECTOR(0 to 7) ;
        INDEX : in INTEGER range 0 to 7;
        OUTPUT : out BIT) ;
end EX_VAR ;
architecture EX_1 of EX_VAR is
begin
  OUTPUT <= A(INDEX) ;
end EX_1 ;
```