

Figure 6-1 Layout of Part of a Programmable Logic Cell Array

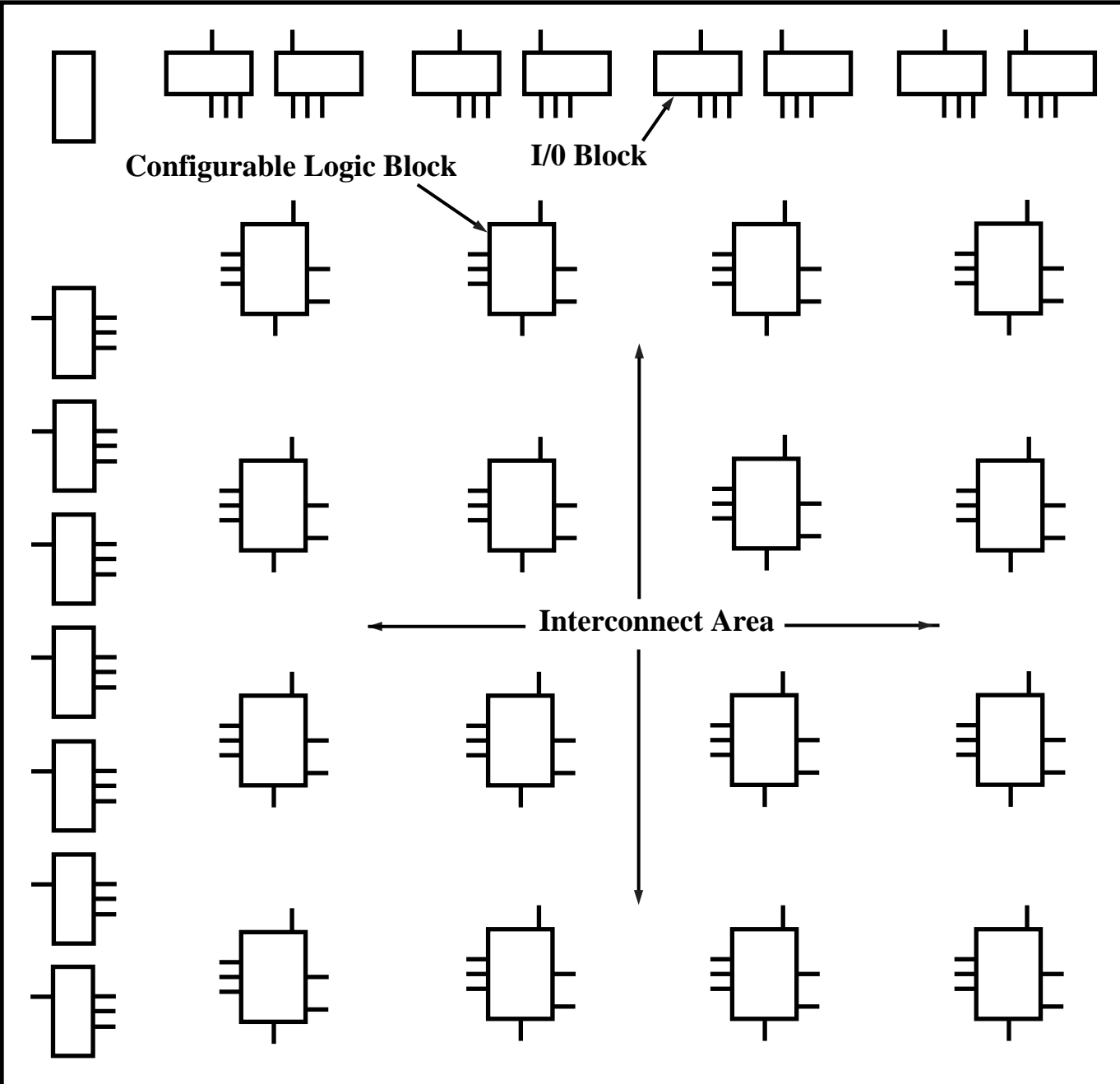


Figure 6-2 Configuration Memory Cell

 


Figure 6-3 Xilinx 3000 Series Logic Cell

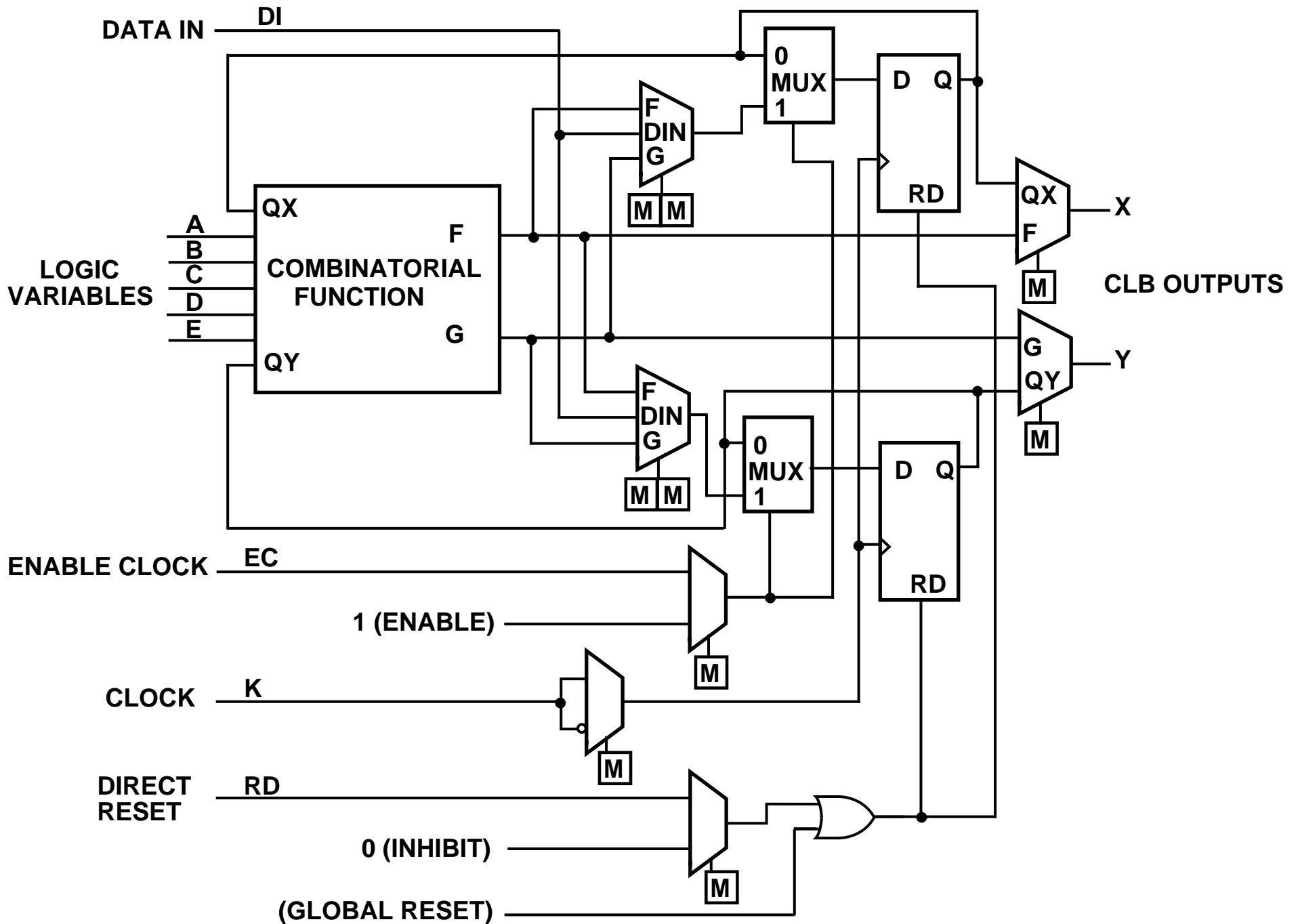


Figure 6-4 Combinatorial Logic Options



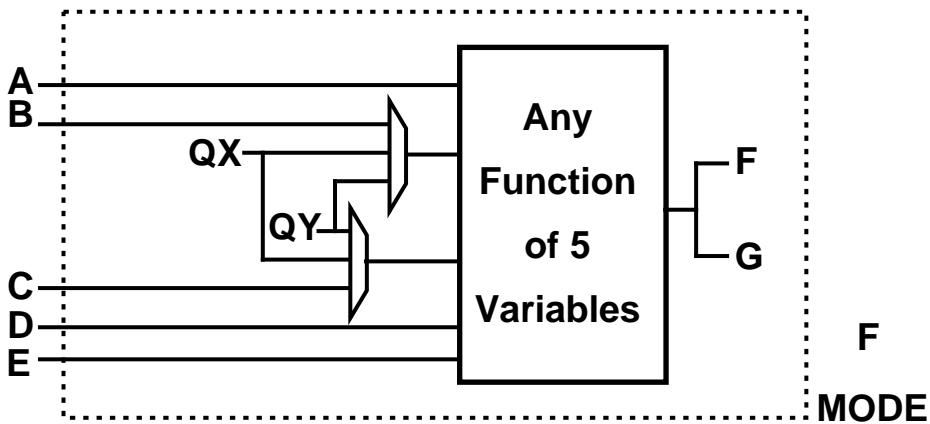
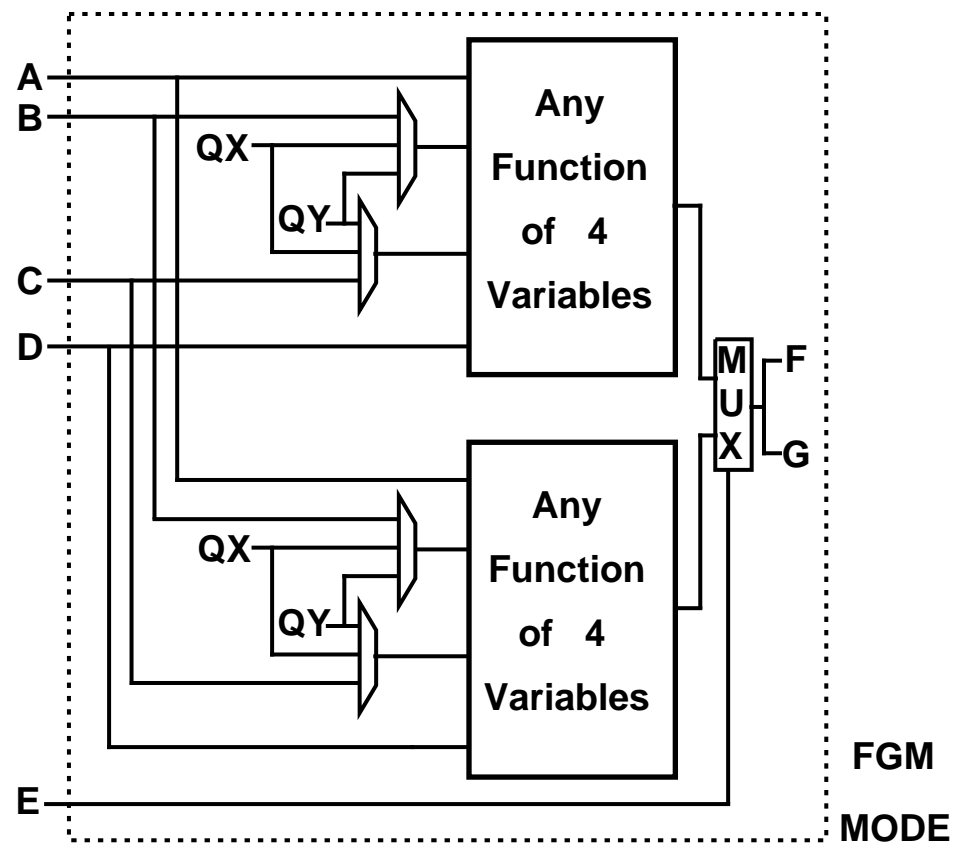
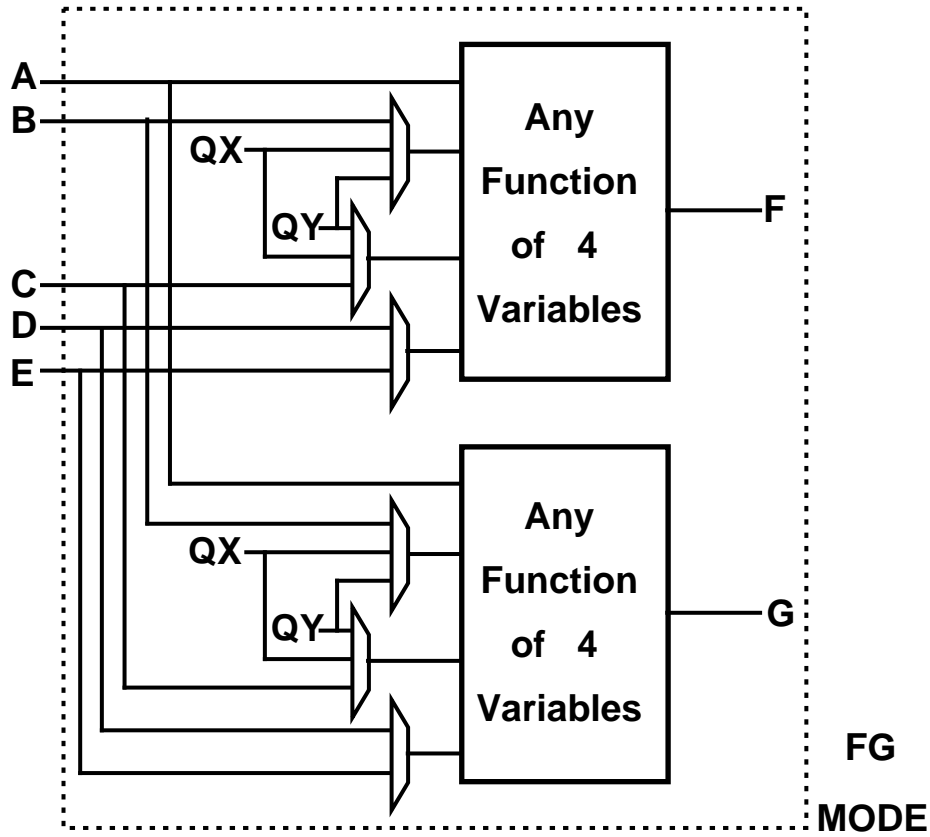


Figure 6-5 Flip-flops with Clock Enable

 

$$Q^+ = EC D1 + EC' Q$$

Figure 6-6 Parallel Adder-Subtractor Logic Cell

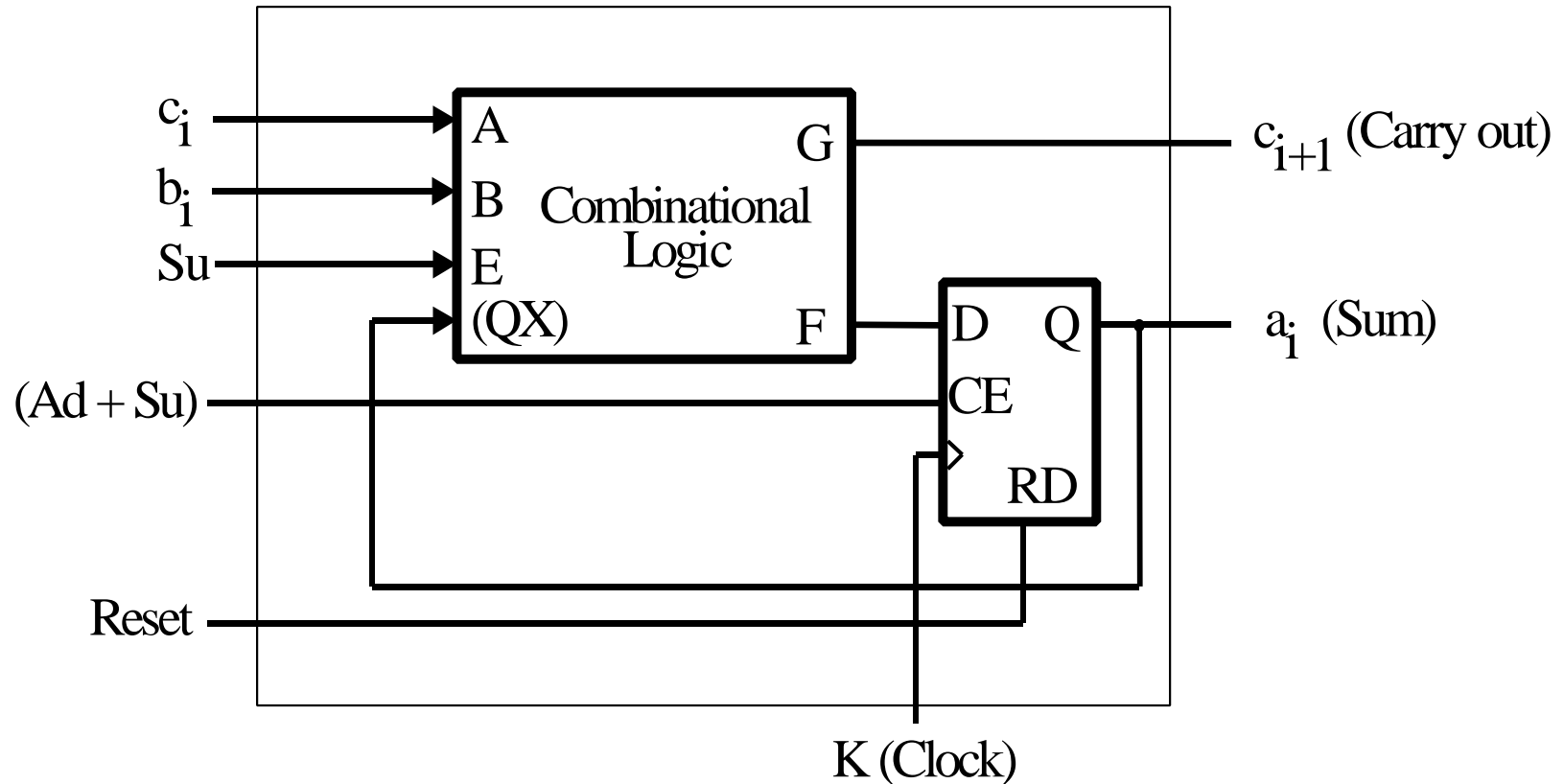

$$F = \text{sum} = a_i + = a_i \oplus (b_i \oplus Su) \oplus c_i$$

$$G = c_{i+1} = \text{carry out} = a_i c_i + (a_i + c_i)(b_i \oplus Su)$$

Figure 6-7 Signal Paths Within Adder-Subtractor Logic Cell



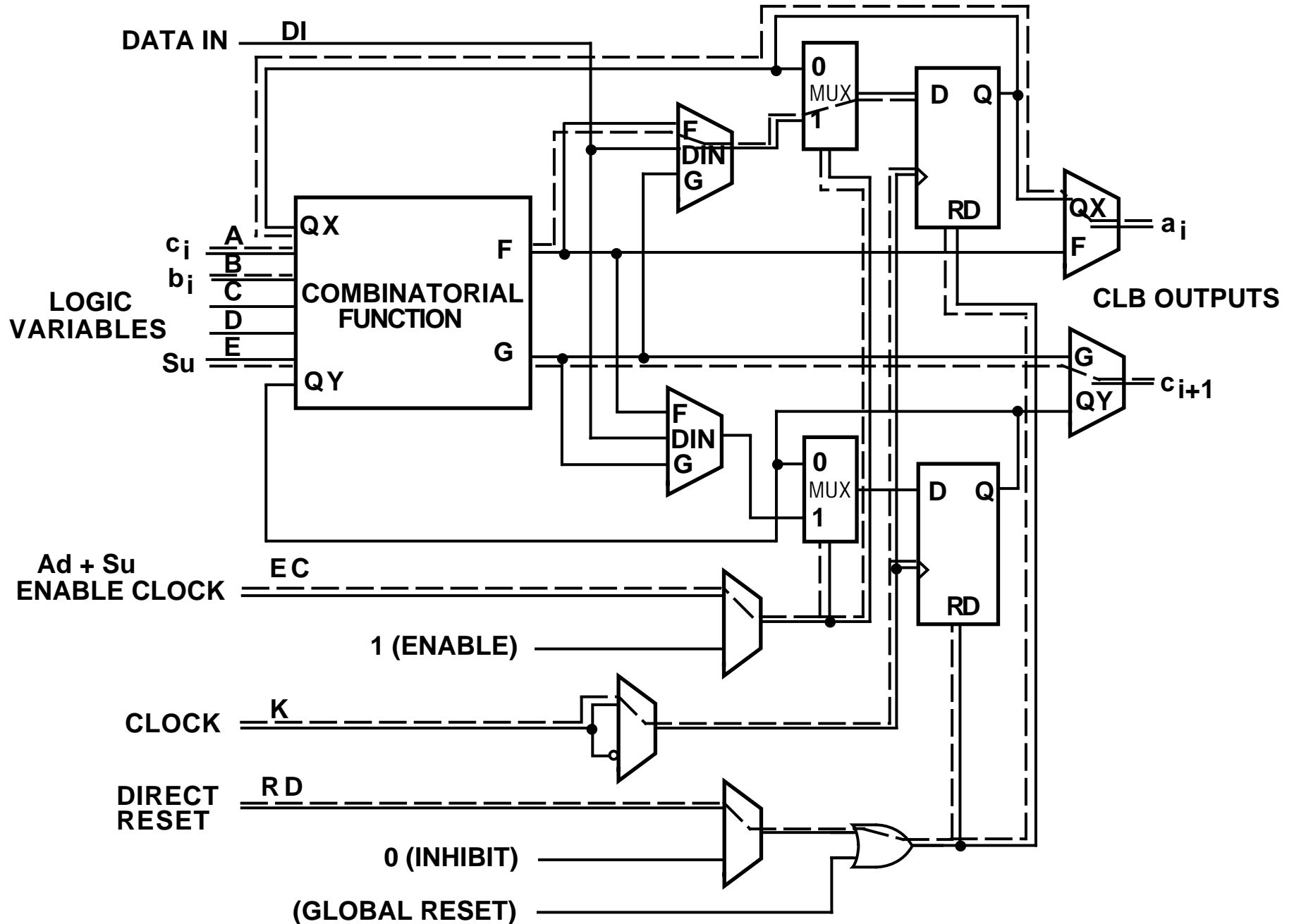


Figure 6-8 Xilinx 3000 Series I/O Block

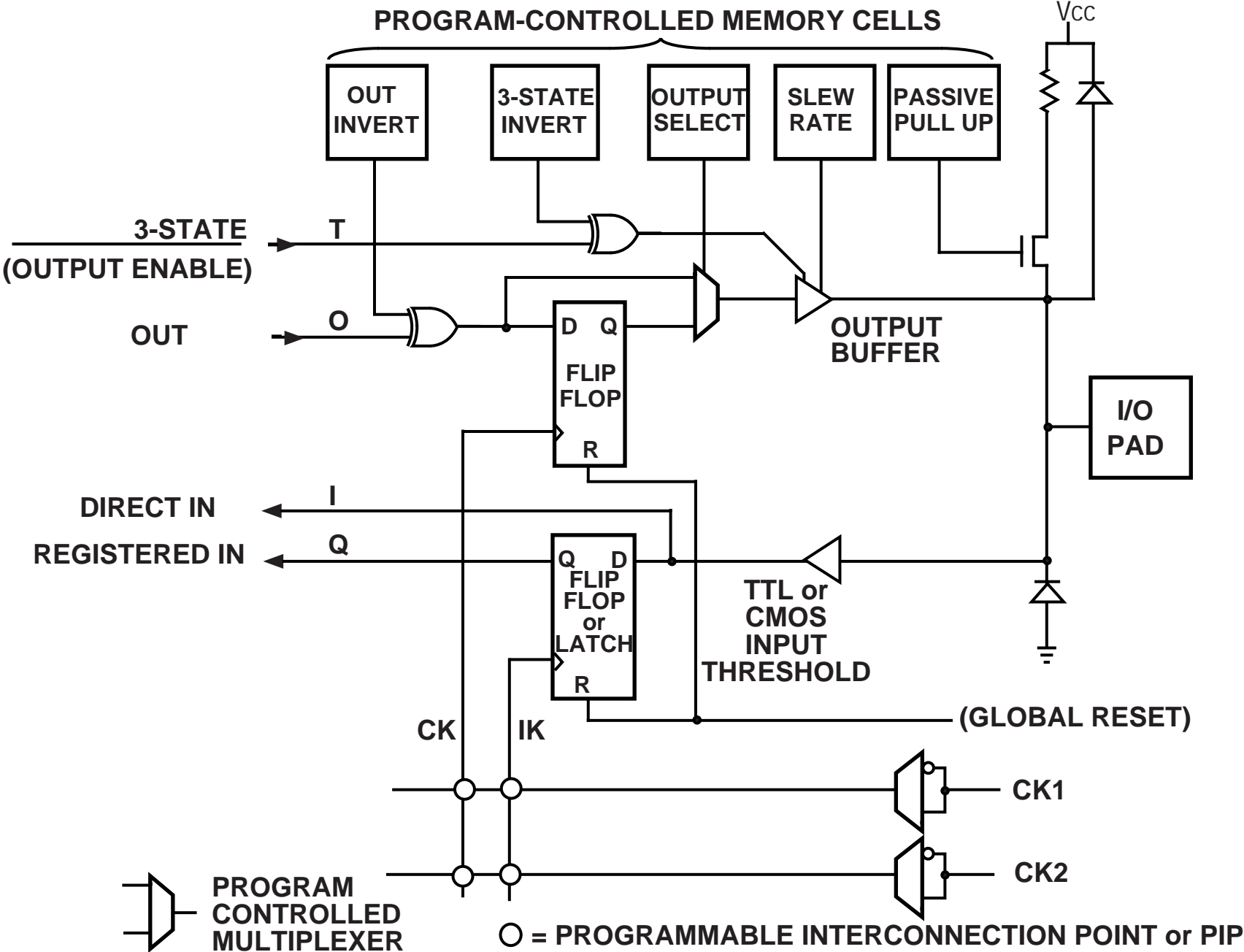

**Figure 6-9
General-purpose
Interconnects**

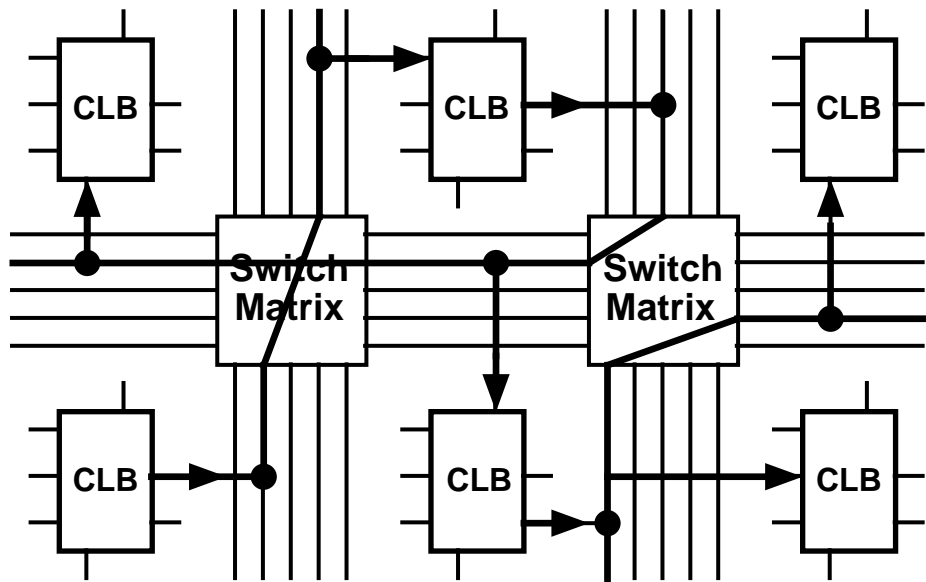

**Figure 6-10
Direct Interconnects
Between Adjacent CLBs**

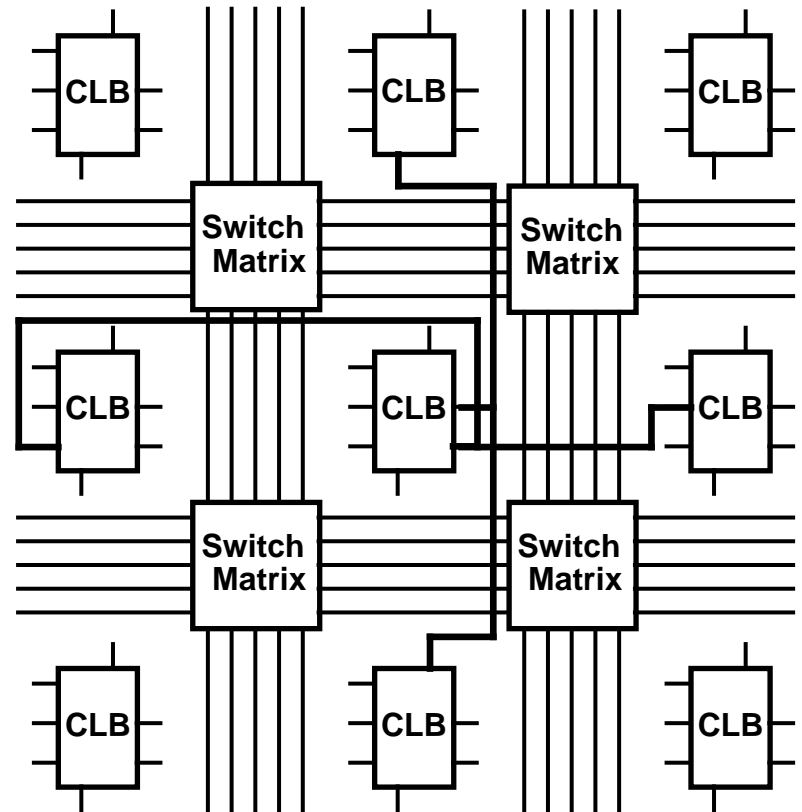


Figure 6-11 Vertical and Horizontal Long Lines



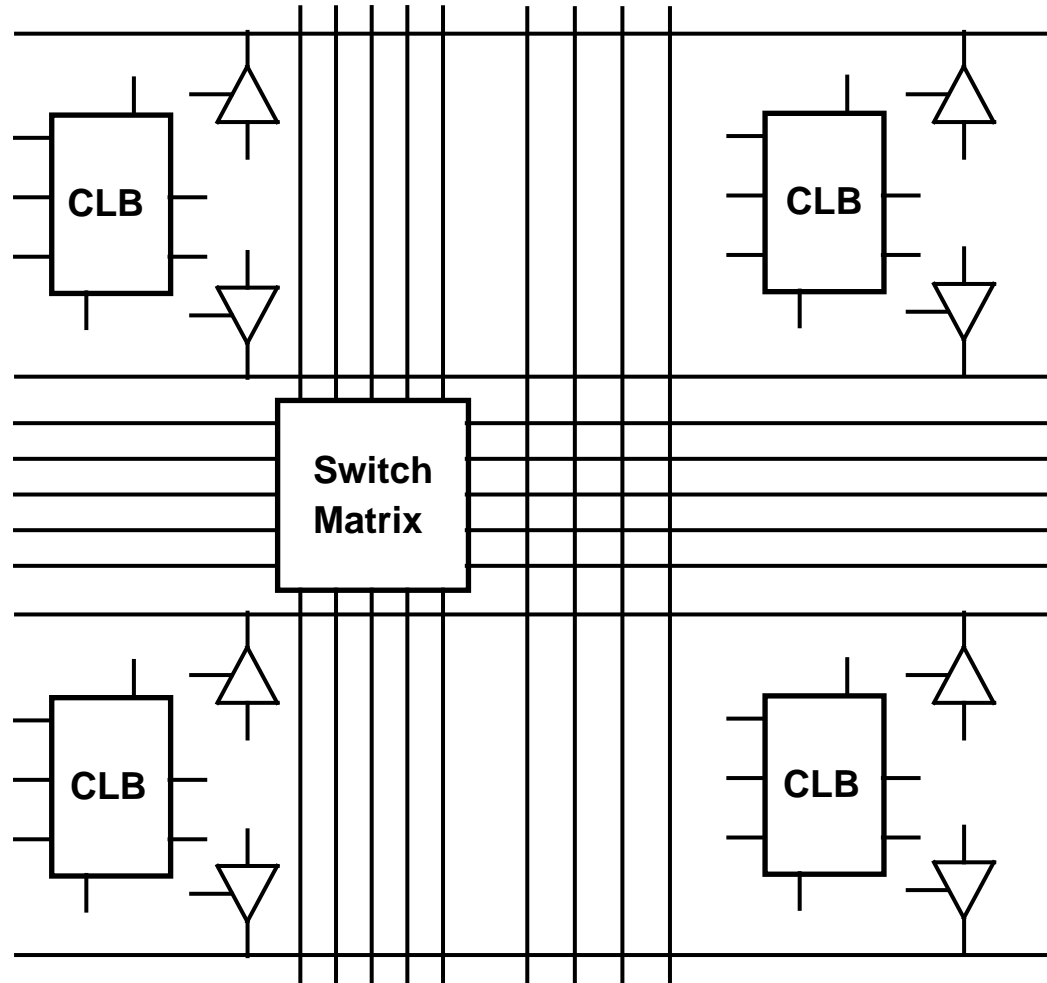


Figure 6-12 Uses of Tristate Buffers

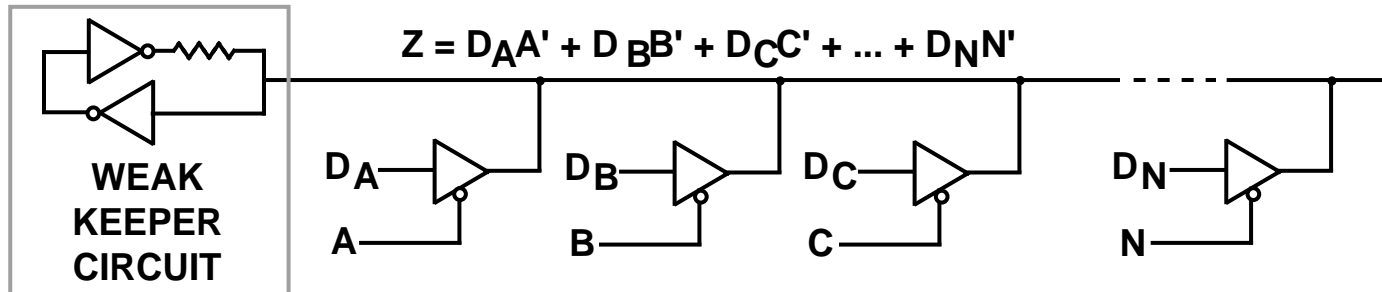


(a) Multiplexer implementation

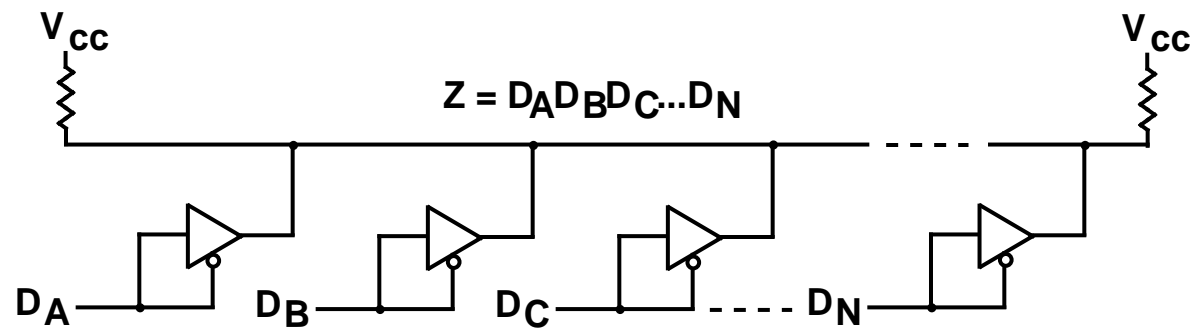

(b) Wired-AND implementation

Figure 6-13 Crystal Oscillator

 


6.2 Designing with FPGAs

Sophisticated CAD tools are available to assist with the design of systems using programmable gate arrays. One method of designing a digital system with a FPGA uses the following steps:

1. Draw a block diagram of the digital system. Define condition and control signals and construct SM charts or state graphs which describe the required sequence of operations.
2. Write a VHDL description of the system. Simulate and debug the VHDL code, and make any necessary corrections to the design which was developed in step 1.
3. Work out the detailed logic design of the system using gates, flip-flops, registers, counters, adders, etc.
4. Enter a logic diagram of the system into the computer using a schematic capture program. Simulate and debug the logic diagram, and make any necessary corrections to the design of step 3.
5. Run a partitioning program. This program will break the logic diagram into pieces which will fit into the configurable logic blocks.
6. Run an automatic place and route program. This will place the logic blocks in appropriate places in the FPGA and then route the interconnections between the logic blocks.
7. Run a program which will generate the bit pattern necessary to program the FPGA.
8. Download the bit pattern into the internal configuration memory cells in the FPGA and test the operation of the FPGA.

Figure 6-14 EPROM Connection for LCA Initialization

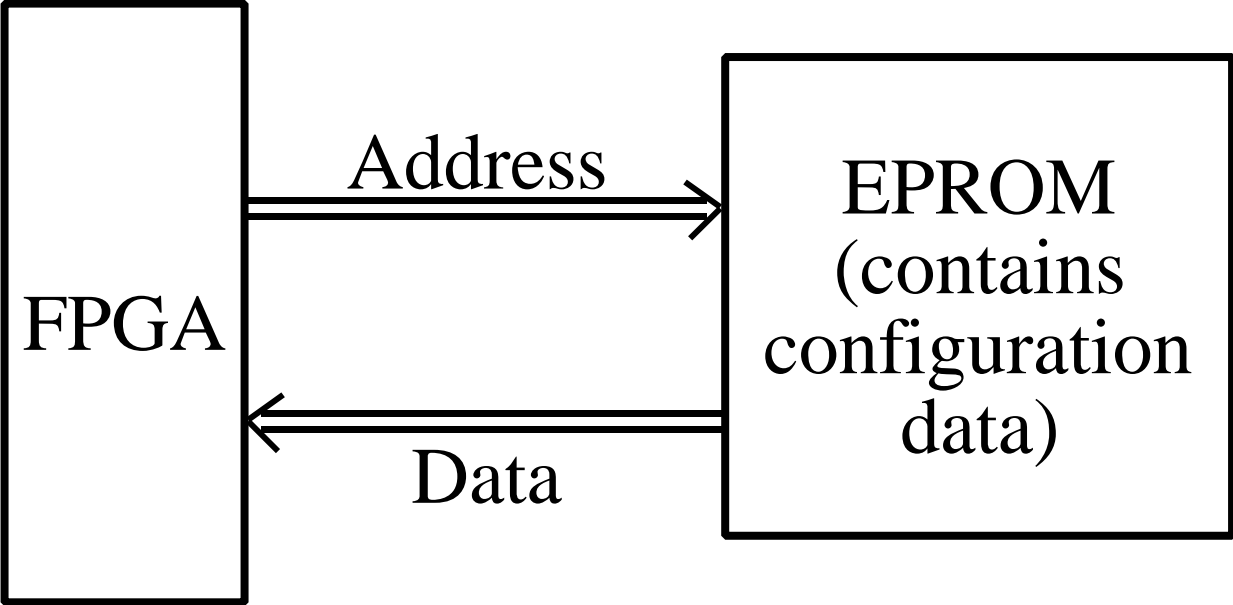

From Page 213

Dice Game Controller Equations (From SM Chart of Figure 5-32)

State Assignment:

T0: AB = 00, T1: AB = 01, T2: AB = 10, T3: AB = 11

$$A^+ = A'B' Dn_roll D711 + A'B' Dn_roll D2312 + A'B Dn_roll Eq + A'B Dn_roll D7 + A Reset'$$

$$B^+ = A'B' Dn_roll D711' + A'B Dn_roll' + A'B Eq' + A B Reset'$$

$$Win = A B'$$

$$Lose = A B$$

$$En_roll = A'$$

$$Sp = A'B' Dn_roll D711' D2312'$$

$$Q^+ = Q' En_roll Rb + Q Rb$$

$$Roll = Q Rb$$

$$Dn_roll = Q Rb'$$

Figure 6-15 Dice Game Block Diagram



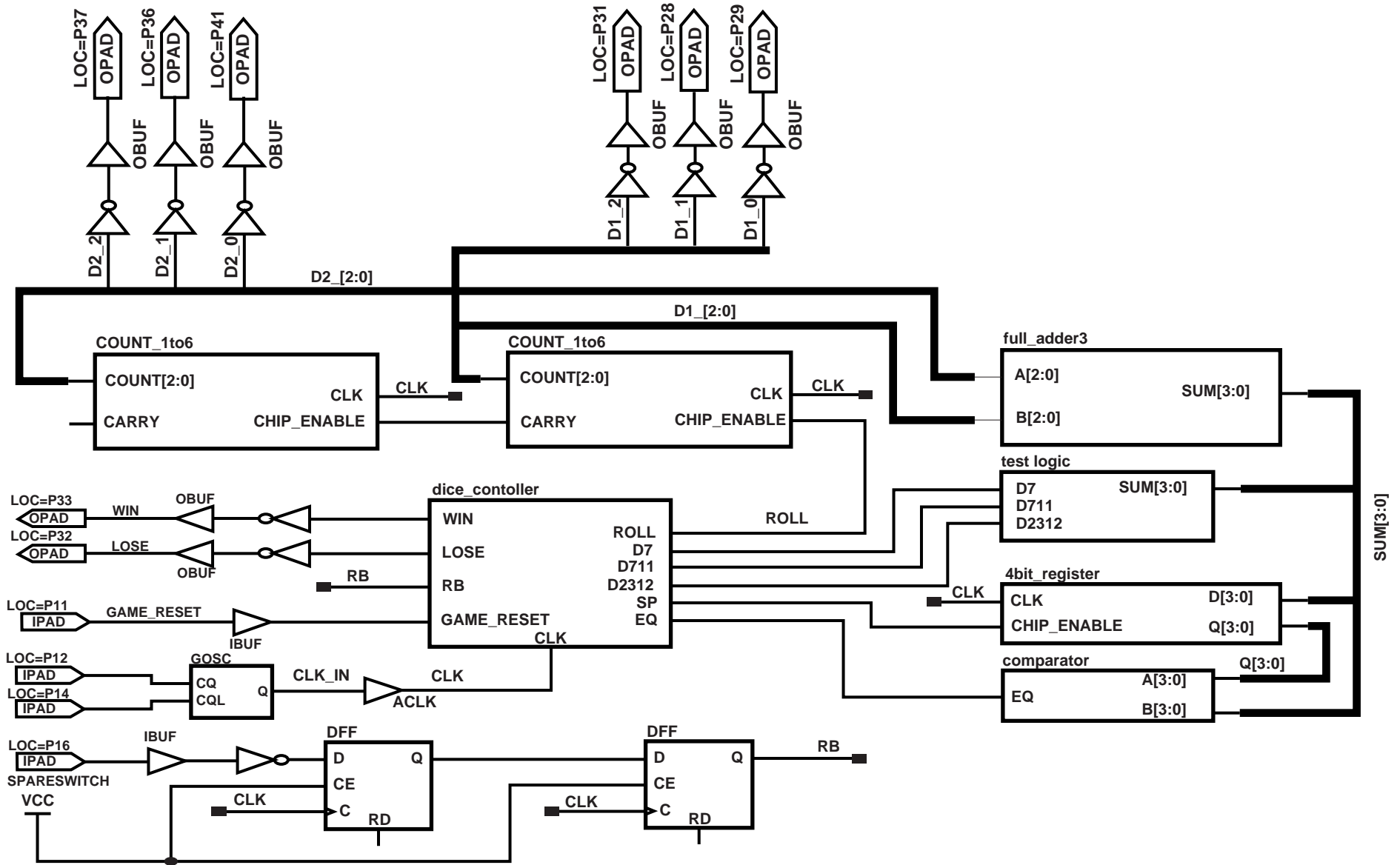


Figure 6-16 Dice Game Controller Module

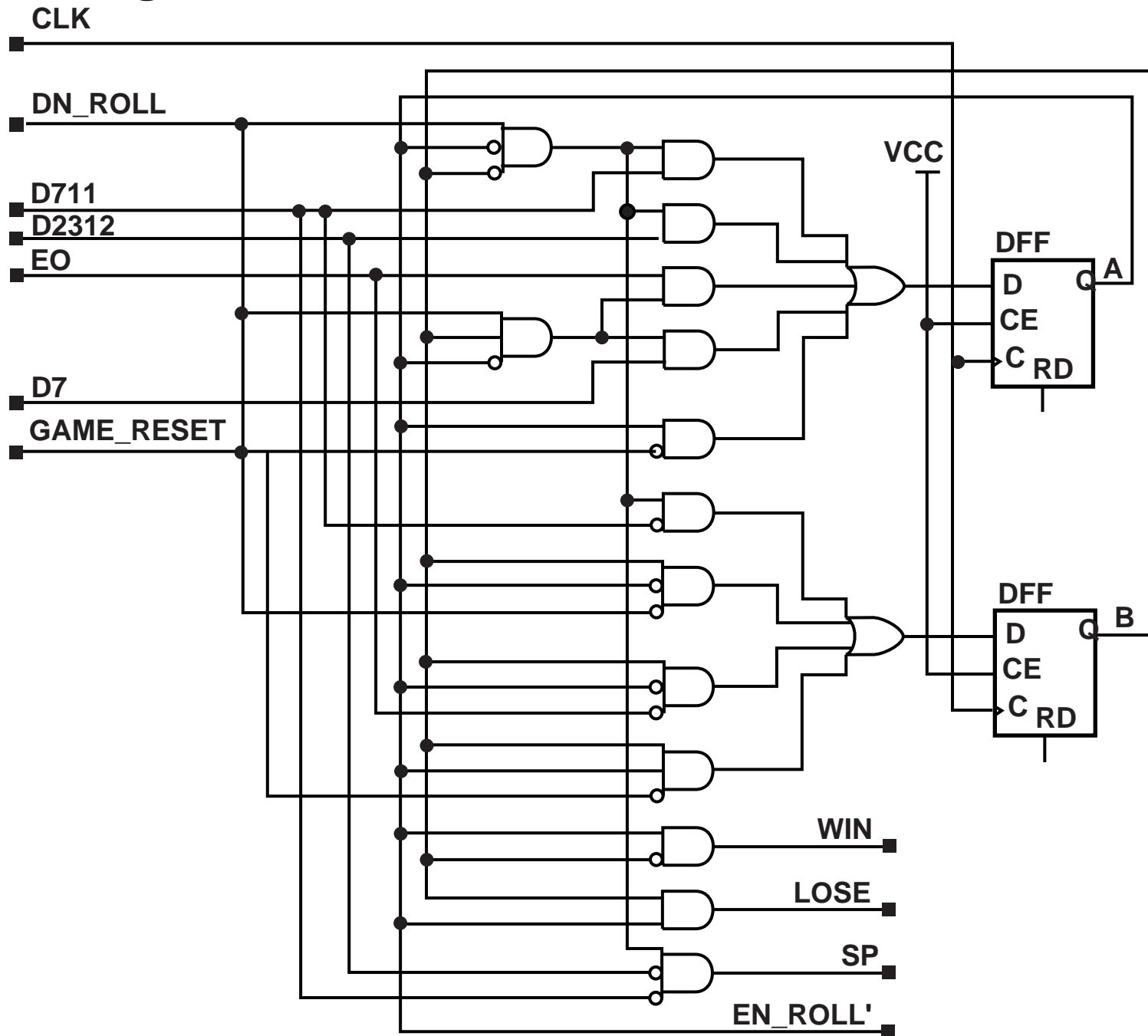

(a) Main controller

Figure 6-16 Dice Game Controller Module

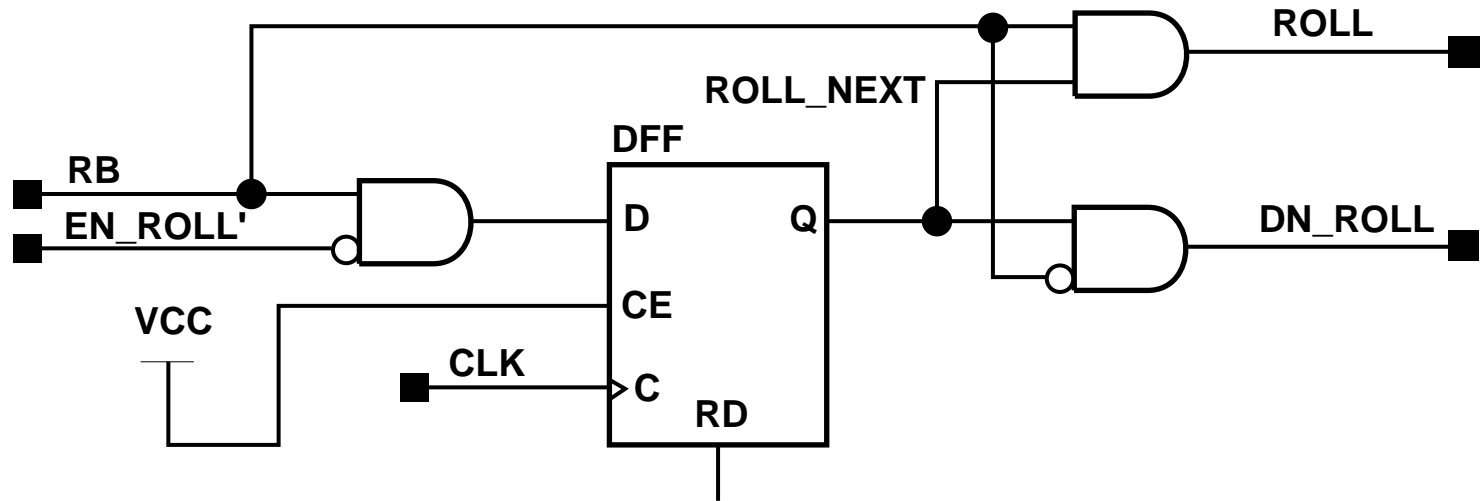

(b) Dice roll controller

Figure 6-17 Modulo-6 Counter

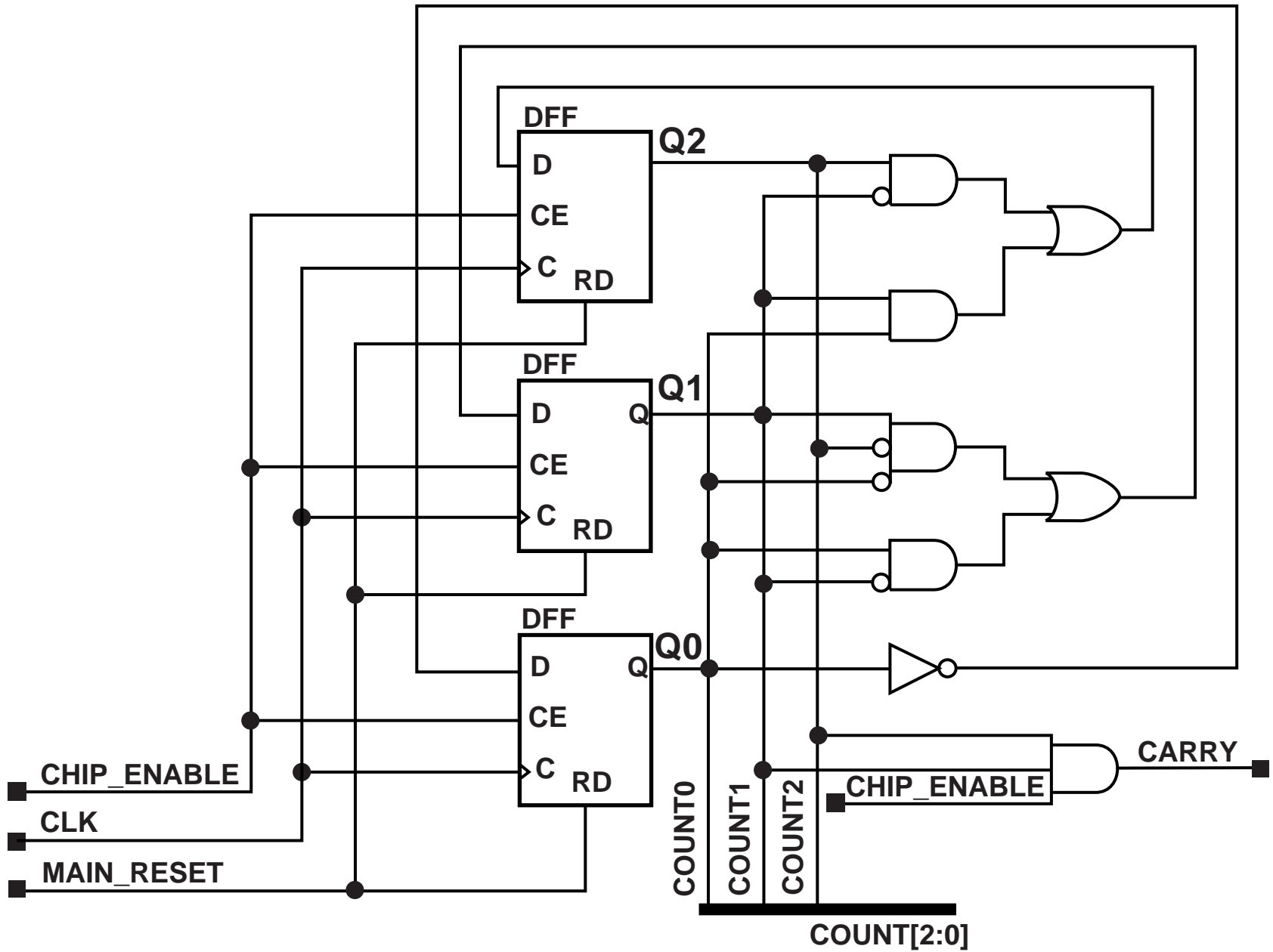


Figure 6-18 Layout and Routing for Dice Game for XC3020

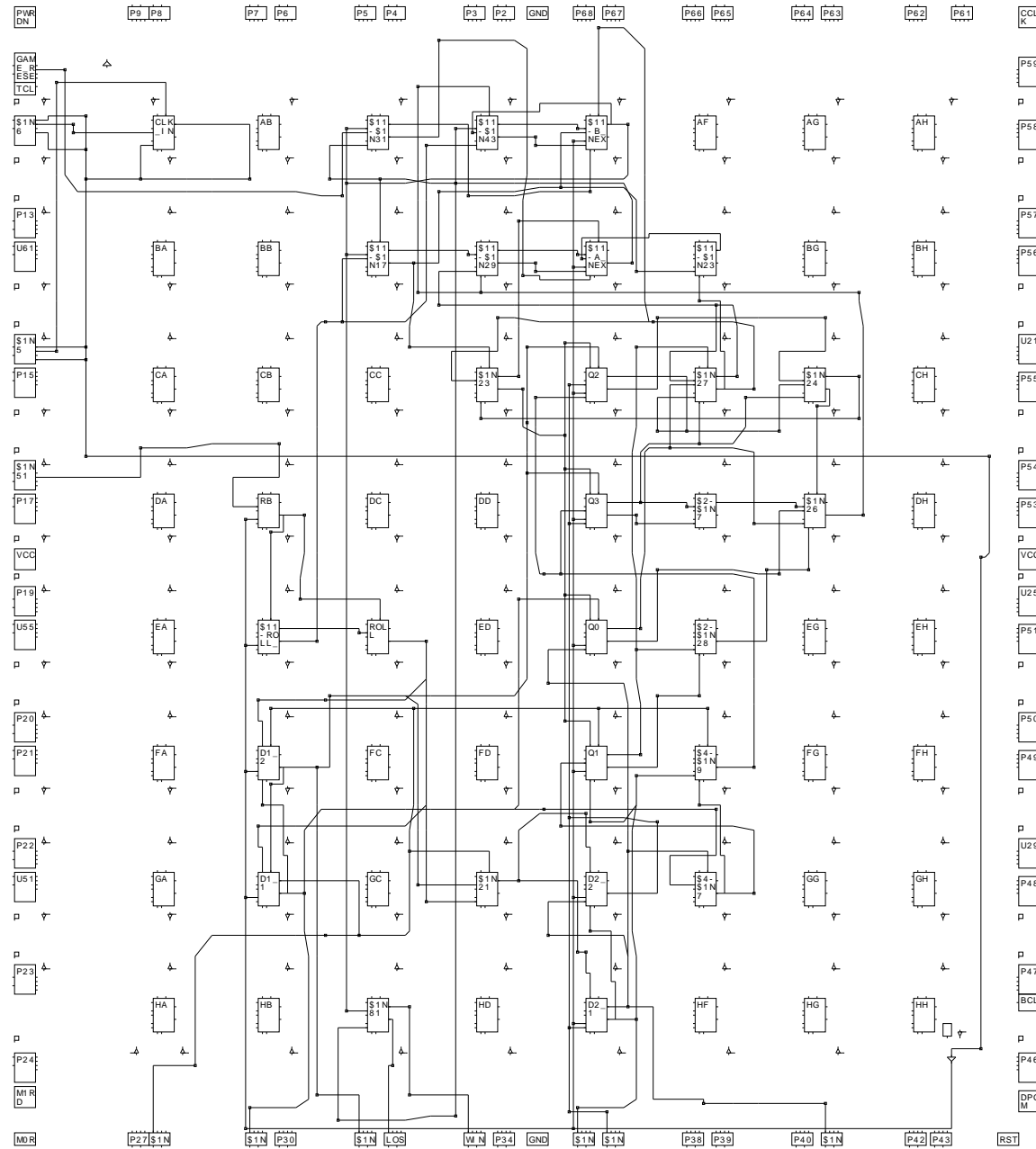


Figure 6-19a Realization of General 6-variable Functions

$$Z(a,b,c,d,e,f) = a'Z(0,b,c,d,e,f) + aZ(1,b,c,d,e,f) = a'Z_0 + aZ_1$$

 


Figure 6-19b Realization of General 7-variable Function

$$\begin{aligned}
 Z(a,b,c,d,e,f,g) &= a'b'Z(0,0,c,d,e,f,g) \\
 &+ a'bZ(0,1,c,d,e,f,g) \\
 &+ ab'Z(1,0,c,d,e,f,g) \\
 &+ abZ(1,1,c,d,e,f,g) \\
 \\
 &= a'b'Y_0 \\
 &+ a'bY_1 \\
 &+ ab'Y_2 \\
 &+ abY_3
 \end{aligned}$$

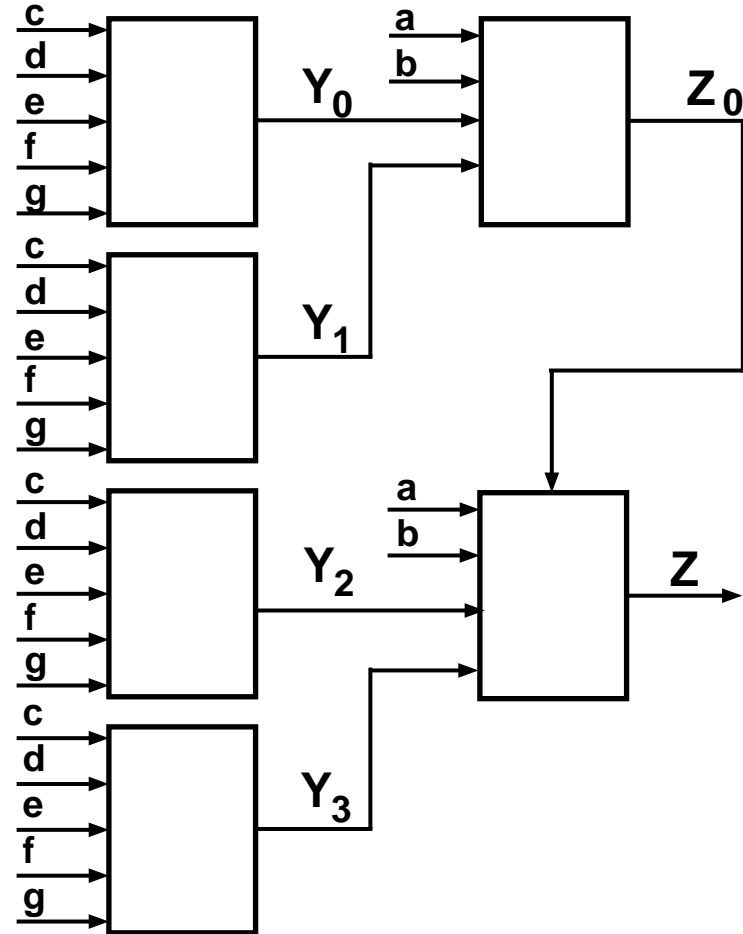


Figure 6-20 Simplified Block Diagram for 4000 Series CLB

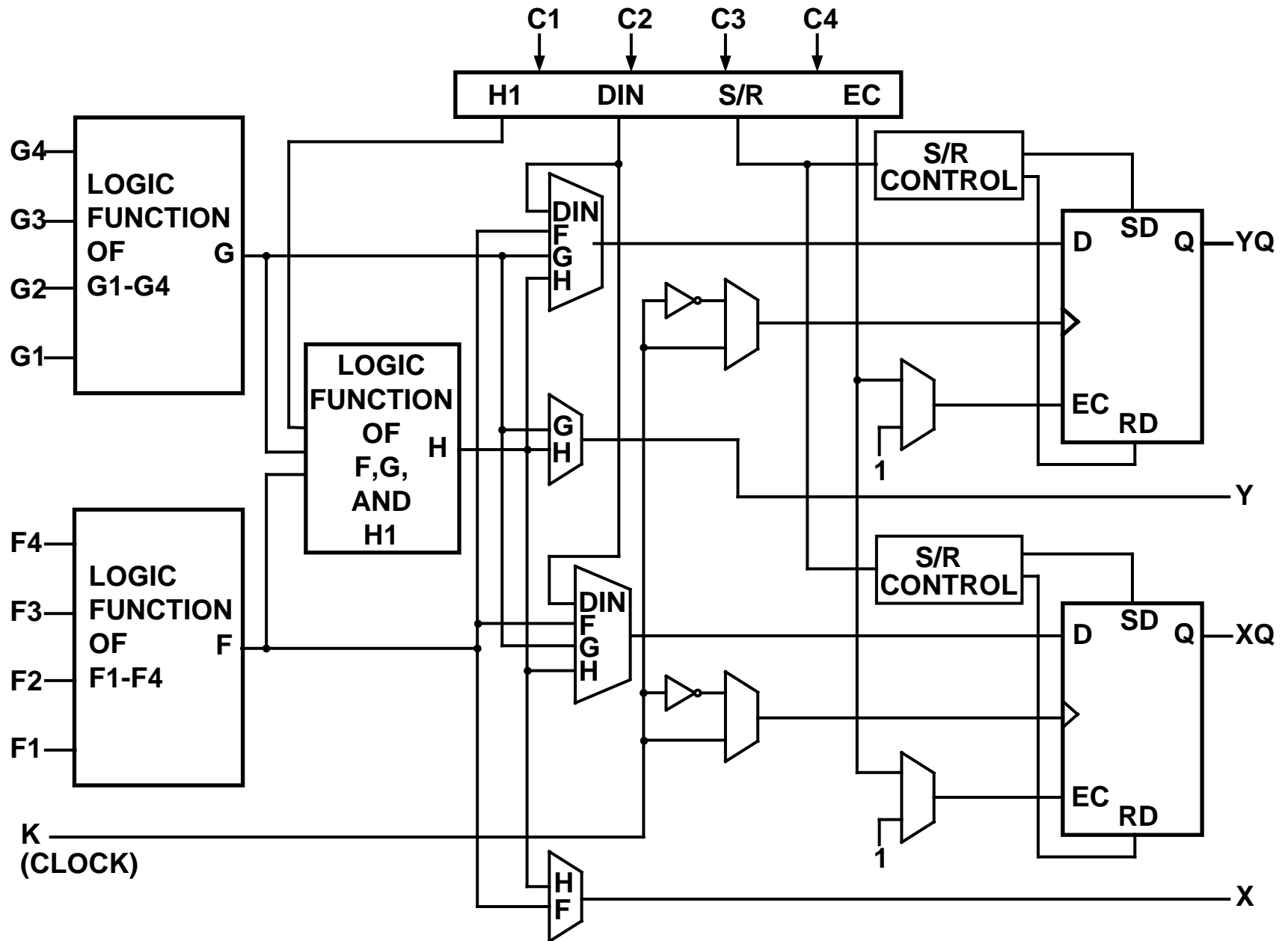


Figure 6-21 XC4000 Dedicated Carry Logic

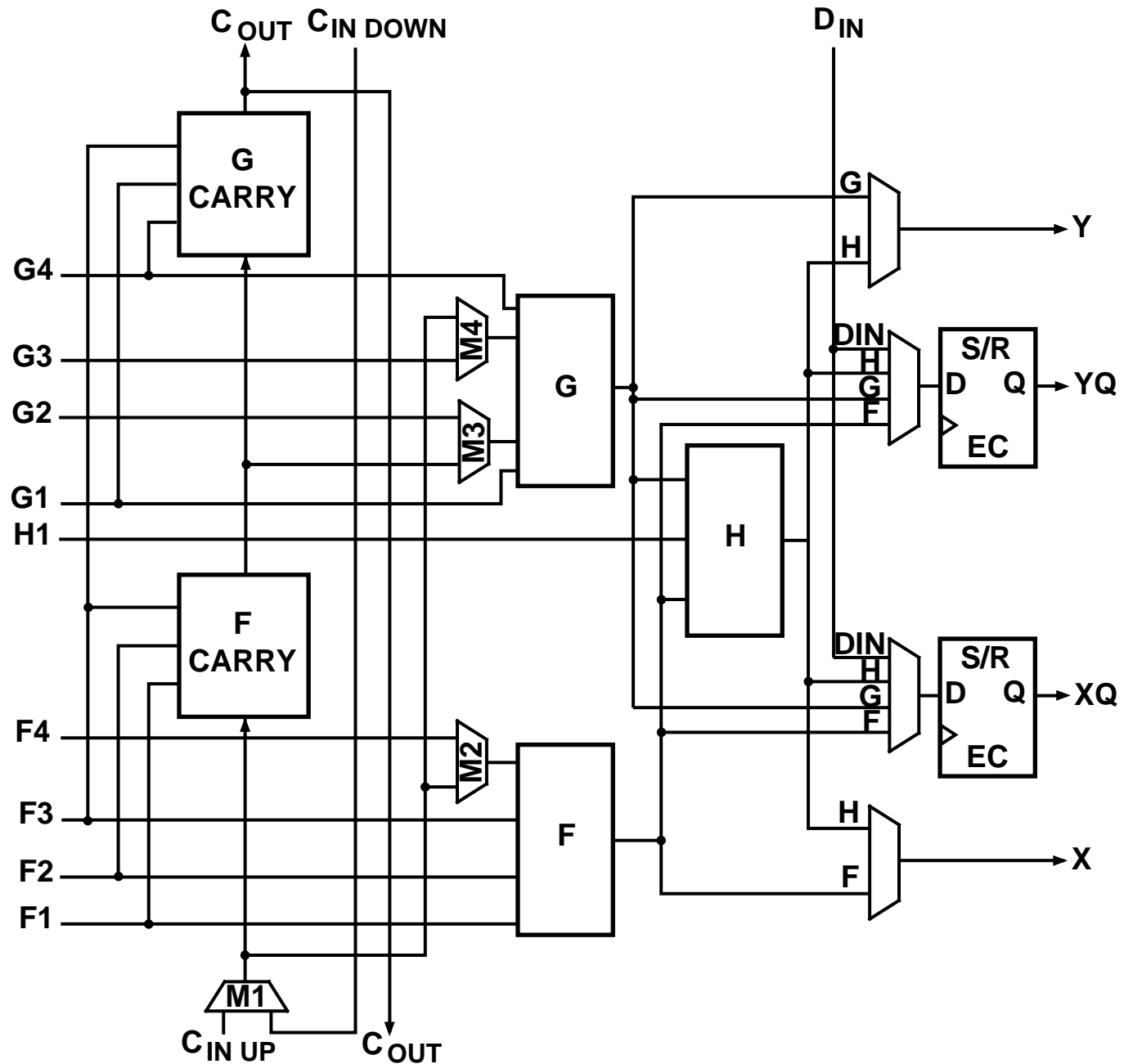


Figure 6-22
Conceptual Diagram of a Typical Addition (2 Bits/CLB)

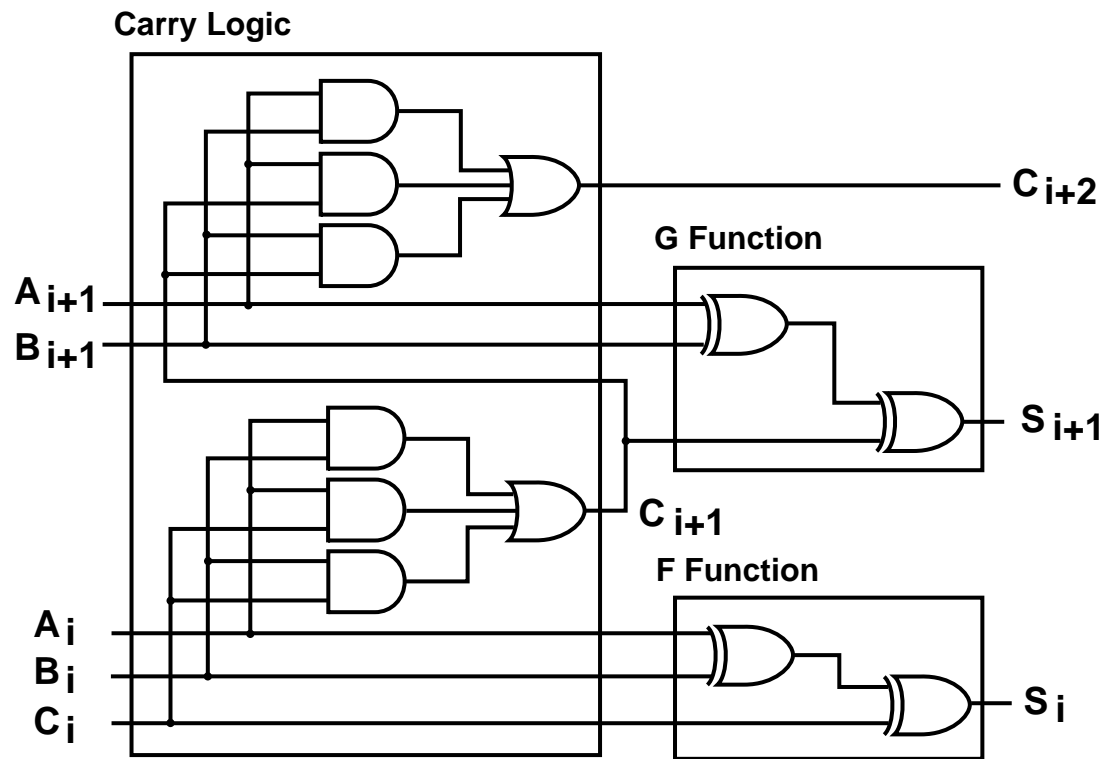


Figure 6-23 Connections for a 4-bit Adder

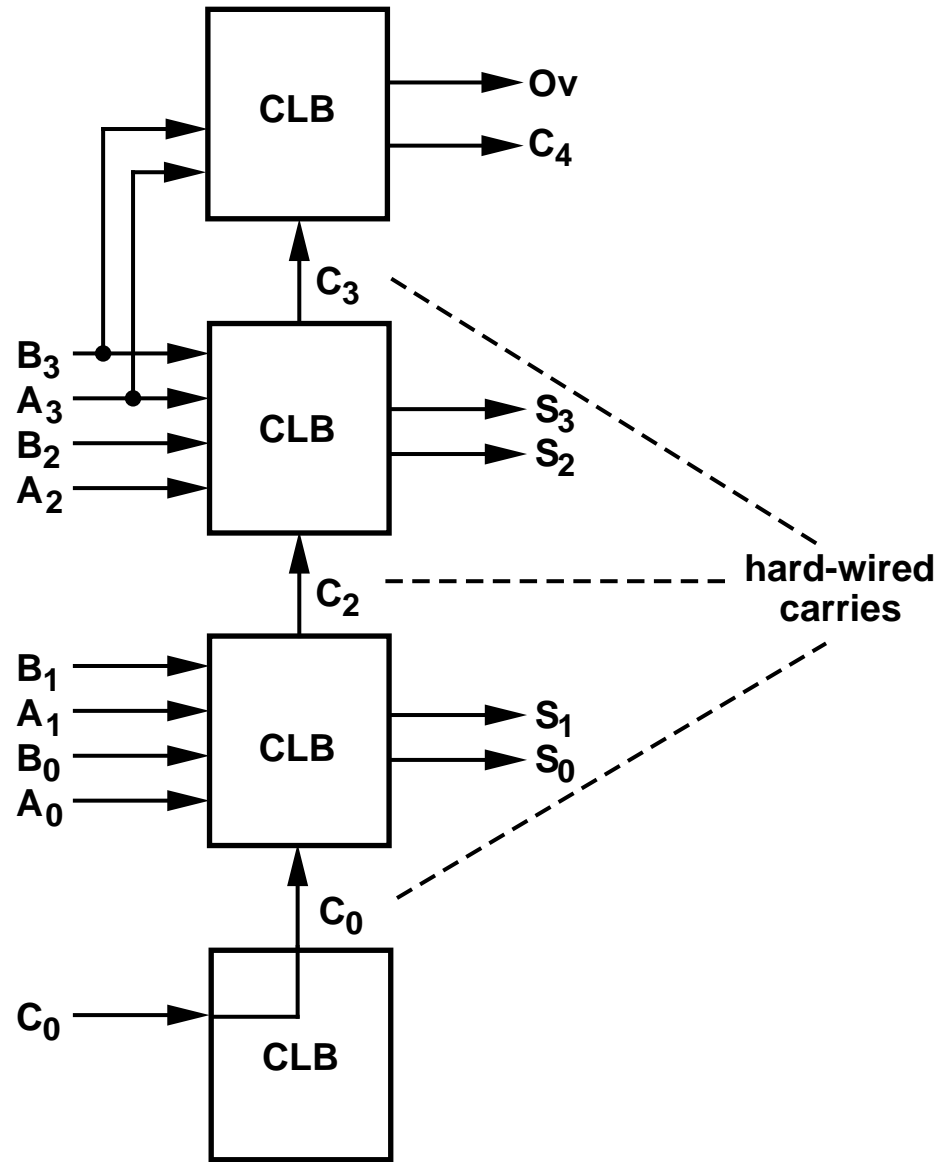


Figure 6-24 CLB as a Read/Write Memory Cell

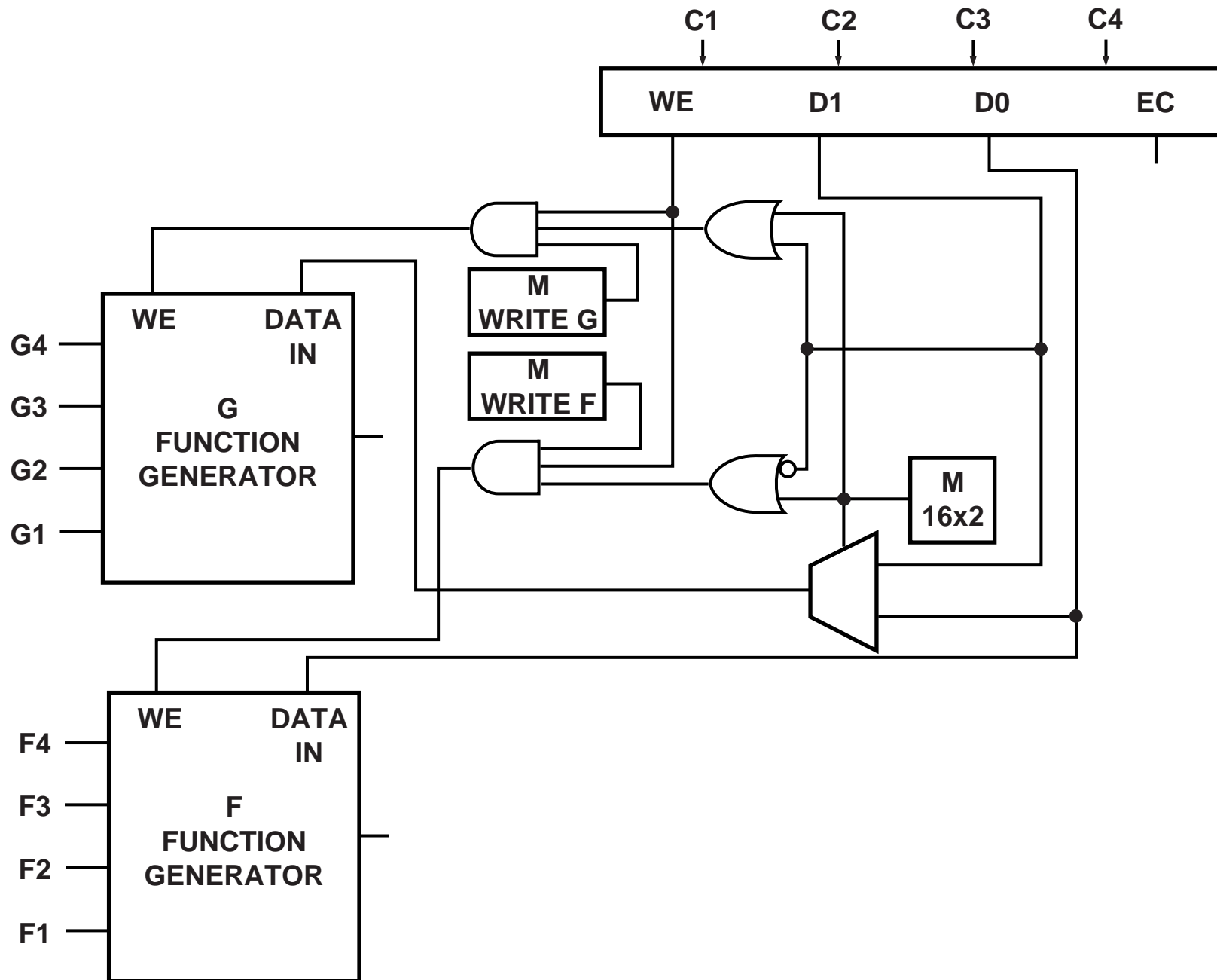


Figure 6-25 4000 Series I/O Block

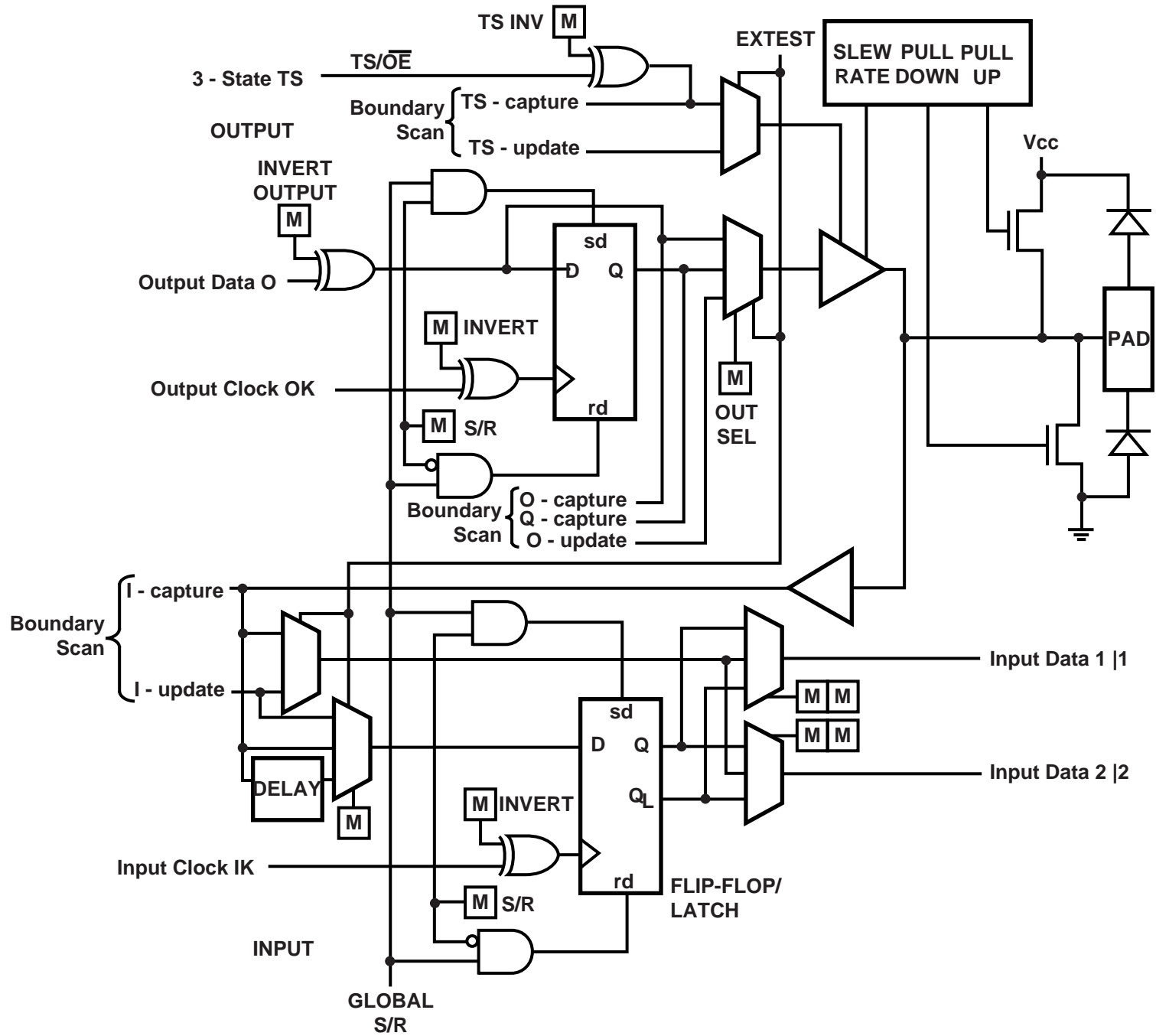


Figure 6-26(a) Behavioral Model for XC4000 CLB

```
library BITLIB;
use BITLIB.bit_pack.all;

entity XC4000CLB is
    port (MEM_BITS : in bit_vector(0 to 51);
          G_IN, F_IN, C_IN : in bit_vector(4 downto 1);
          K : in bit; Y,X : out bit; Q : out bit_vector (1 downto 0));
end XC4000CLB;

architecture behavior of XC4000CLB is
    alias G_FUNC : bit_vector(0 to 15) is MEM_BITS(0 to 15);
    alias F_FUNC : bit_vector(0 to 15) is MEM_BITS(16 to 31);
    alias H_FUNC : bit_vector(0 to 7) is MEM_BITS(32 to 39);
    type bv2D is array (1 downto 0) of bit_vector(1 downto 0);
    constant FF_SEL : bv2D := (MEM_BITS(40 to 41),MEM_BITS(42 to 43));
    alias Y_SEL : bit is MEM_BITS(44); alias X_SEL : bit is MEM_BITS(45);
    alias EDGE_SEL: bit_vector(1 downto 0) is MEM_BITS(46 to 47);
    alias EC_SEL : bit_vector(1 downto 0) is MEM_BITS(48 to 49);
    alias SR_SEL : bit_vector(1 downto 0) is MEM_BITS(50 to 51);
    alias H1 : bit is C_IN(1); alias DIN : bit is C_IN(2);
    alias SR : bit is C_IN(3); alias EC : bit is C_IN(4);

    -- Timing spec for XC4000, Speed Grade -4
    constant Tiho : TIME := 6 ns;           -- F/G inputs to X/Y outputs via H
    constant Tilo : TIME := 4 ns;          -- F/G inputs to X/Y outputs
    constant Tcko : TIME := 3 ns;          -- Clock K to Q outputs
    constant Trio : TIME := 7 ns;          -- S/R to Q outputs
    signal G,F,H : bit;
```

Figure 6-26(b) Behavioral Model for XC4000 CLB

begin

G <= G_FUNC (vec2int(G_IN)); F <= F_FUNC (vec2int(F_IN));

H <= H_FUNC (vec2int(H1&G&F)) **after** (Tiho-Tilo);

X <= (X_SEL **and** H) **or** (**not** X_SEL **and** F) **after** Tilo;

Y <= (Y_SEL **and** H) **or** (**not** Y_SEL **and** G) **after** Tilo;

process (K, SR)

-- update FF outputs

variable DFF_EC,D : bit_vector(1 **downto** 0);

begin

for i **in** 0 **to** 1 **loop**

DFF_EC(i) := EC **or** EC_SEL(i);

case FF_SEL(i) **is**

when "00" => D(i) := DIN; **when** "01" => D(i) := F;

when "10" => D(i) := G; **when** "11" => D(i) := H;

end case;

if (SR='1') **then** Q(i)<=SR_SEL(i) **after** Trio;-- If SR set, then set or reset ff

else

if (DFF_EC(i)='1') **then**

-- If clock enabled then

-- If correct triggering edge then update ff value

if ((EDGE_SEL(i)='1' **and** rising_edge(K)) **or** (EDGE_SEL(i)='0'

and falling_edge(K))) **then** Q(i)<=D(i) **after** Tcko; **end if;**

end if;

end if;

end loop;

end process;

end behavior;

Table 6-1 Truth Tables for G and F Function Generators

G4	G3	G2	G1	G	F4	F3	F2	F1	F
K	M	Q1	Q0	Q1 ⁺	St	M	Q1	Q0	Q0 ⁺
0	0	0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	0	1	1
0	0	1	0	0	0	0	1	0	1
0	0	1	1	0	0	0	1	1	0
0	1	0	0	0	0	1	0	0	0
0	1	0	1	1	0	1	0	1	0
0	1	1	0	0	0	1	1	0	1
0	1	1	1	0	0	1	1	1	0
1	0	0	0	0	1	0	0	0	1
1	0	0	1	1	1	0	0	1	1
1	0	1	0	1	1	0	1	0	1
1	0	1	1	0	1	0	1	1	0
1	1	0	0	0	1	1	0	0	1
1	1	0	1	1	1	1	0	1	0
1	1	1	0	1	1	1	1	0	1
1	1	1	1	0	1	1	1	1	0

Figure 6-27 XC4000 Implementation of Multiplier Control

entity Fig_4_6 **is**

port (St, K, M, CLK : **in** bit; Ad, Sh, Load, Done : **out** bit);
end Fig_4_6;

architecture CLBs **of** Fig_4_6 **is**

component XC4000CLB

port(MEM_BITS : **in** bit_vector(0 **to** 51);
 G_IN, F_IN, C_IN : **in** bit_vector(4 **downto** 1);
 K : **in** bit; Y,X : **out** bit; Q : **out** bit_vector (1 **downto** 0));

end component;

constant MEM1 : bit_vector (0 **to** 51) :=

 "0000010001100110011000101110101000000000100100110000";

constant MEM2 : bit_vector (0 **to** 51) :=

 "000100010001000100000000100010000000000000000000110000";

constant MEM3 : bit_vector (0 **to** 51) :=

 "000000000010001000110011000100010000000000000000110000";

signal Q : bit_vector (1 **downto** 0);

signal G_IN1,G_IN2,G_IN3,F_IN1,F_IN2,F_IN3 : bit_vector (3 **downto** 0);

begin

 G_IN1<=K&M&Q; F_IN1<=St&M&Q; G_IN2<="00"&Q; F_IN2<=St&'0'&Q;
 G_IN3<=M&'0'&Q; F_IN3<=M&'0'&Q;


 CLB1: XC4000CLB **port map** (MEM1,G_IN1,F_IN1,"1000",CLK,**open**,**open**,Q);

 CLB2: XC4000CLB **port map** (MEM2,G_IN2,F_IN2,"1000",CLK,Done,Load,**open**);

 CLB3: XC4000CLB **port map** (MEM3,G_IN3,F_IN3,"1000",CLK,Ad,Sh,**open**);

end CLBs;

Figure 6-28 Partial State Graph

 

One-hot state assignment for flip-flops Q0 Q1 Q2 Q3:

T0: 1000, T1: 0100, T2: 0010, T3: 0001

$$Q3^+ = X1 Q0 + X2 Q1 + X3 Q2 + X4 Q3$$

$$Z1 = X1 Q0 + X3 Q2$$

$$Z2 = X2 Q1 + X4 Q3$$

Figure 6-29 Altera 7000 Series Architecture for EPM7032, 7064, and 7096 Devices

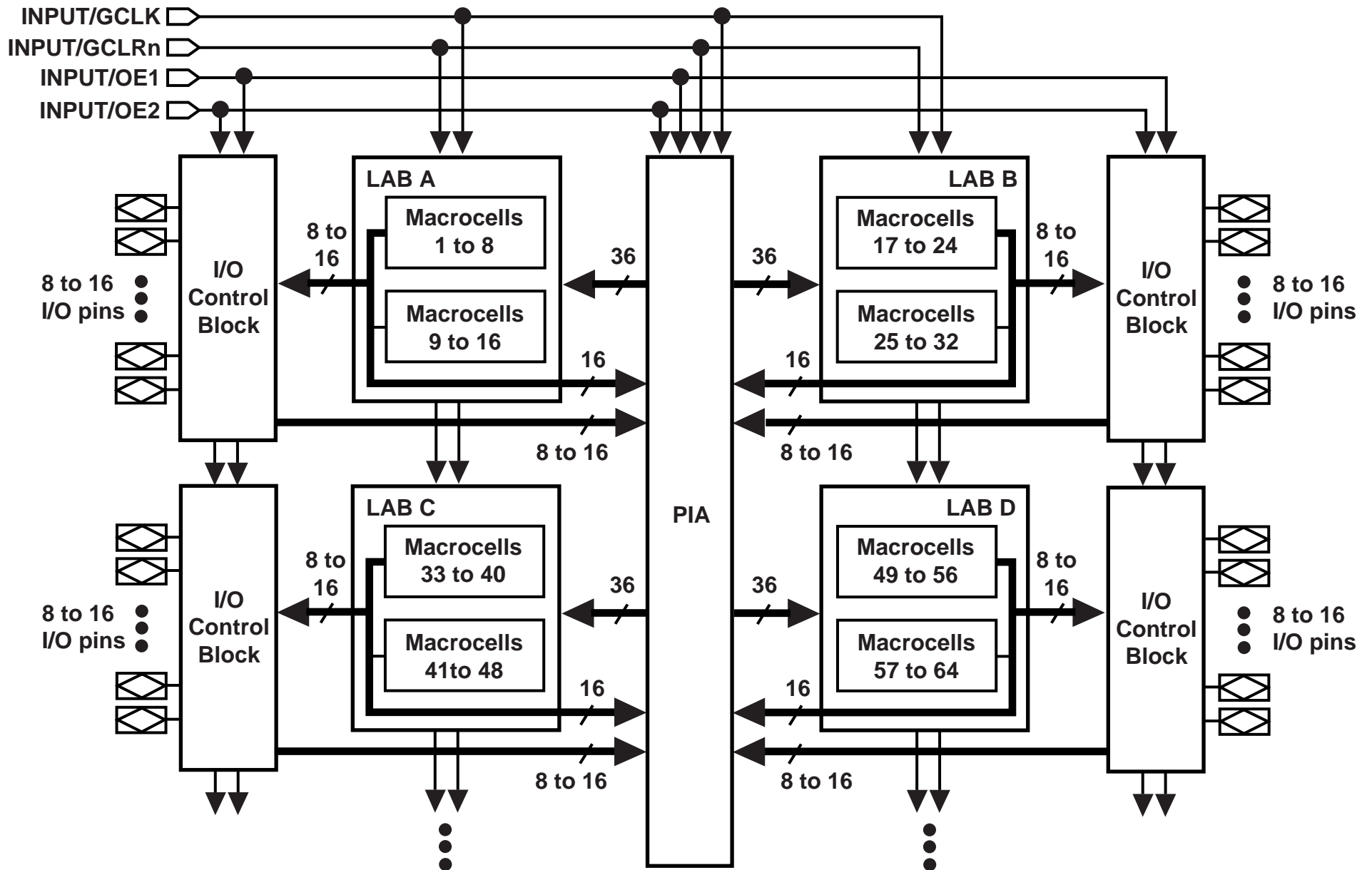


Figure 6-30

Macrocell for EMP7032, 7064, and 7096 Devices

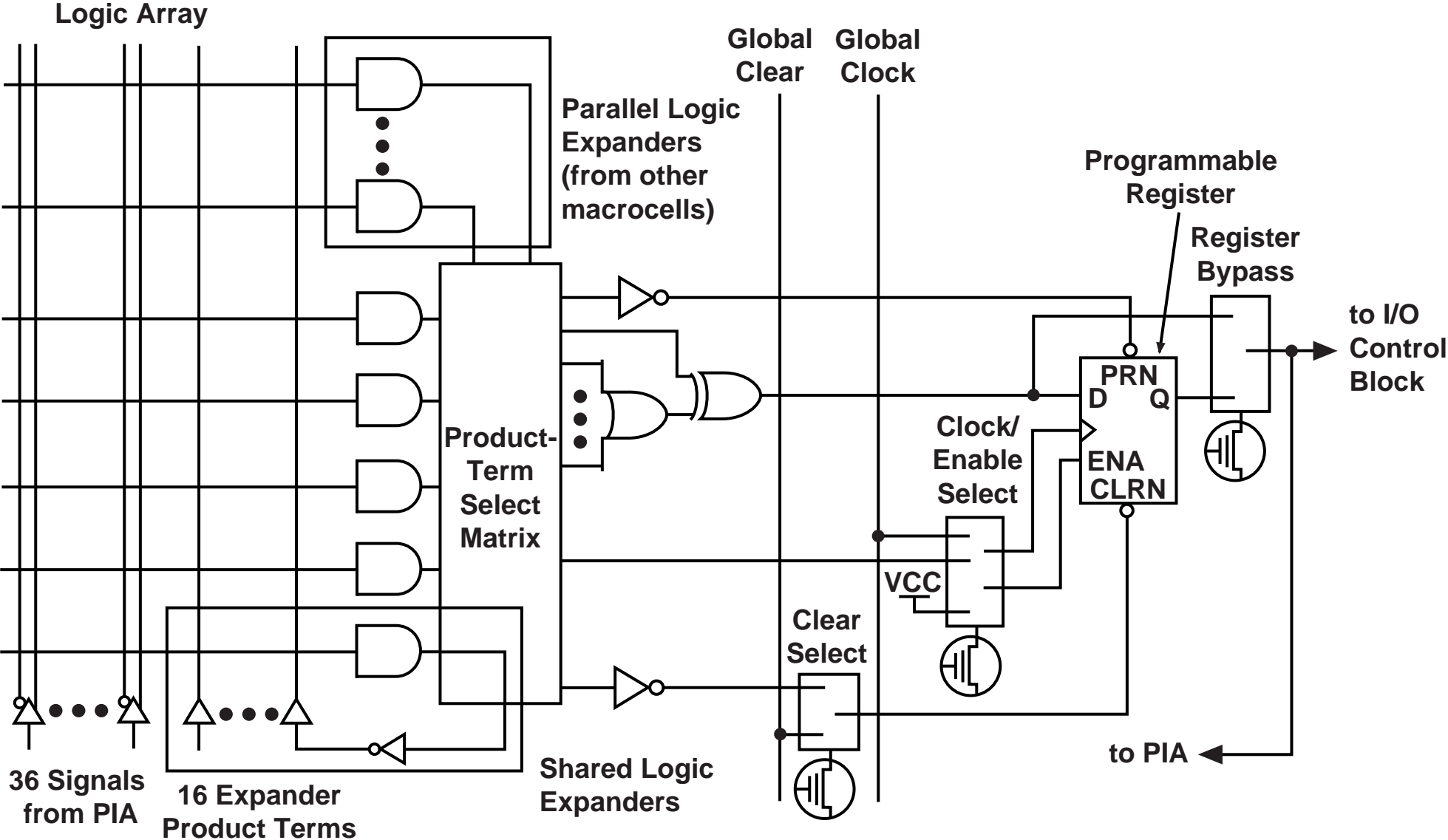


Figure 6-31 Sharable Expanders

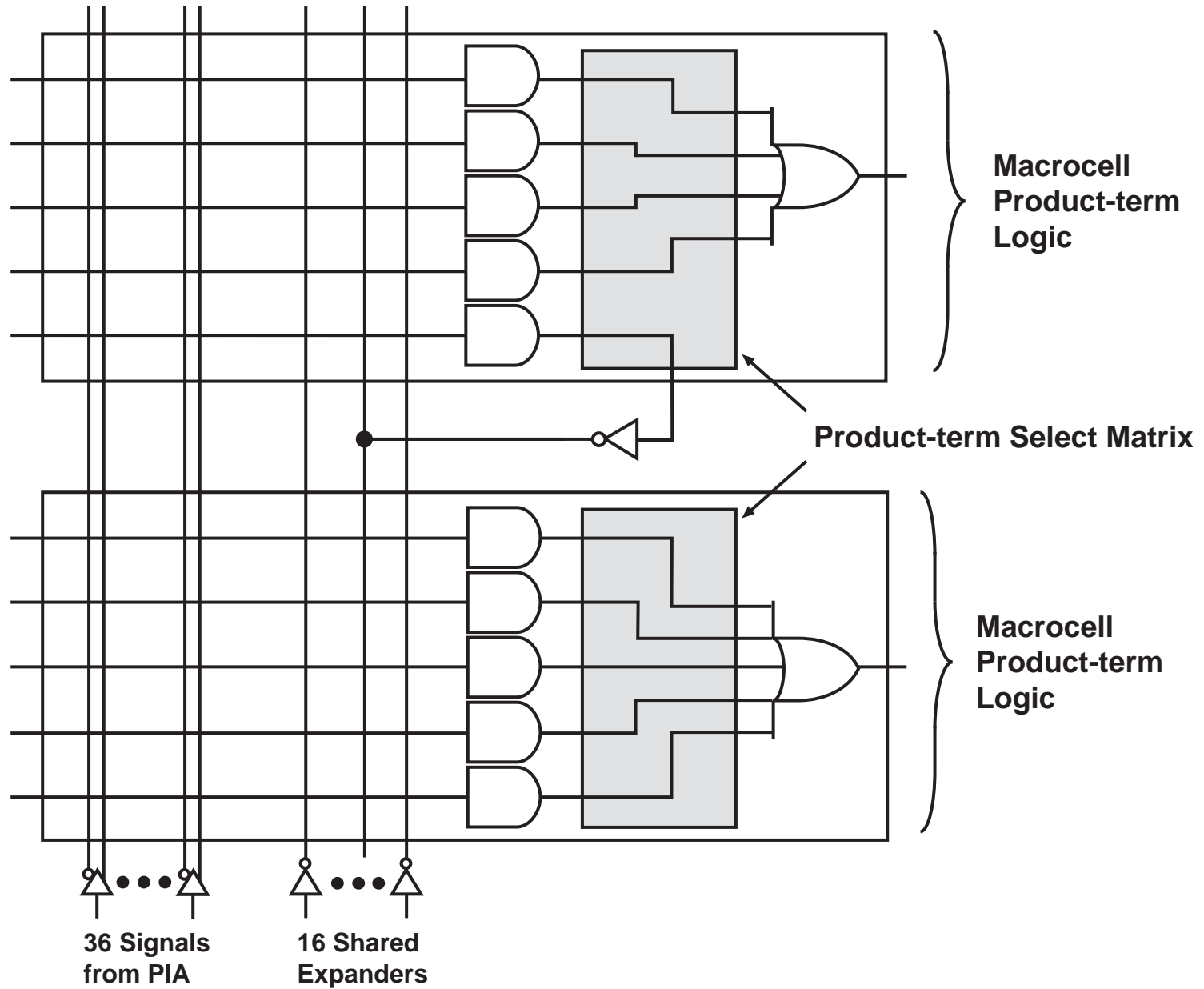


Figure 6-32 Parallel Expanders

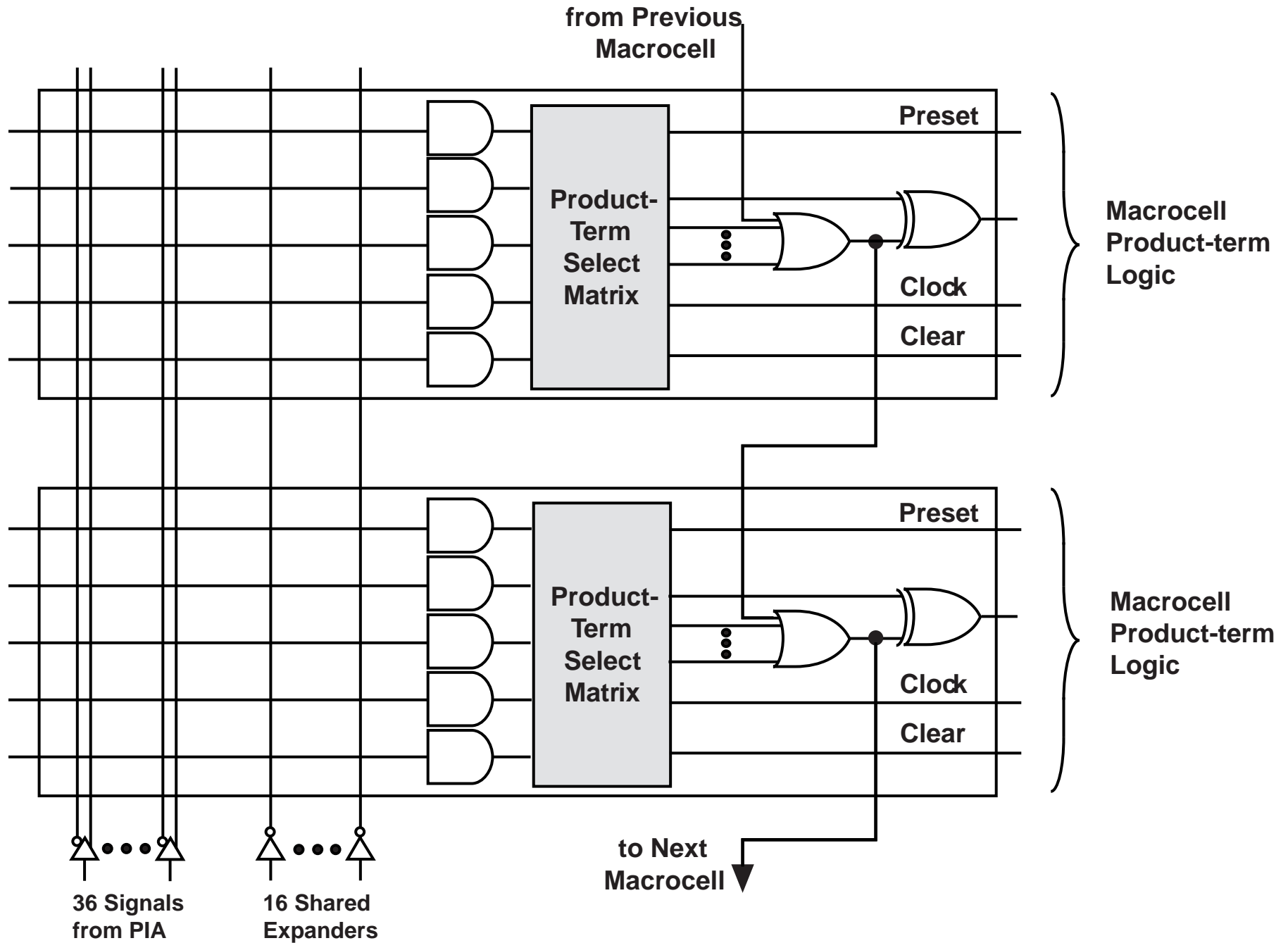


Figure 6-33 I/O Block for EPM7032, 7064, and 7096

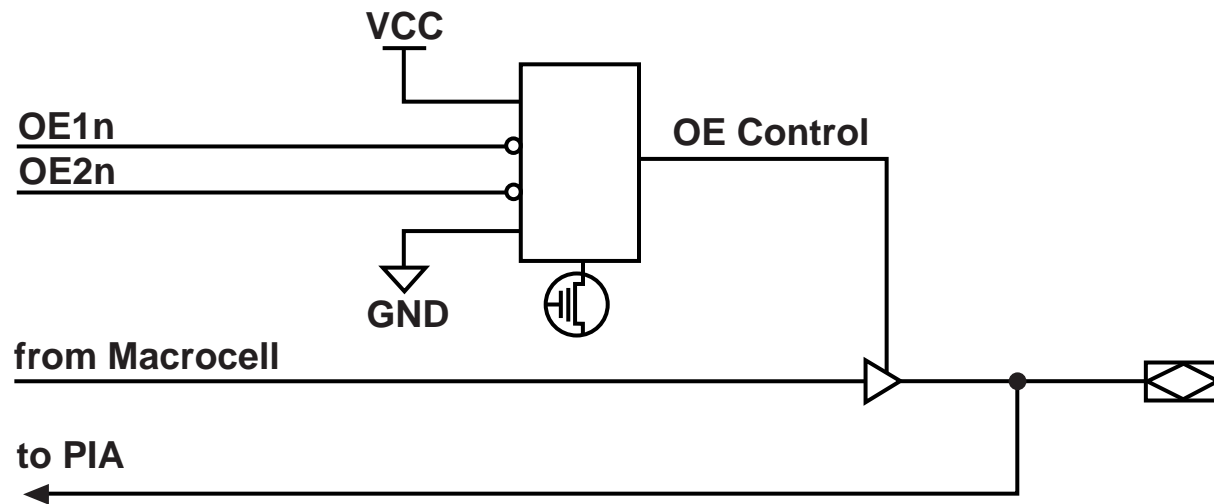


Figure 6-34 FLEX 10K Device Block Diagram

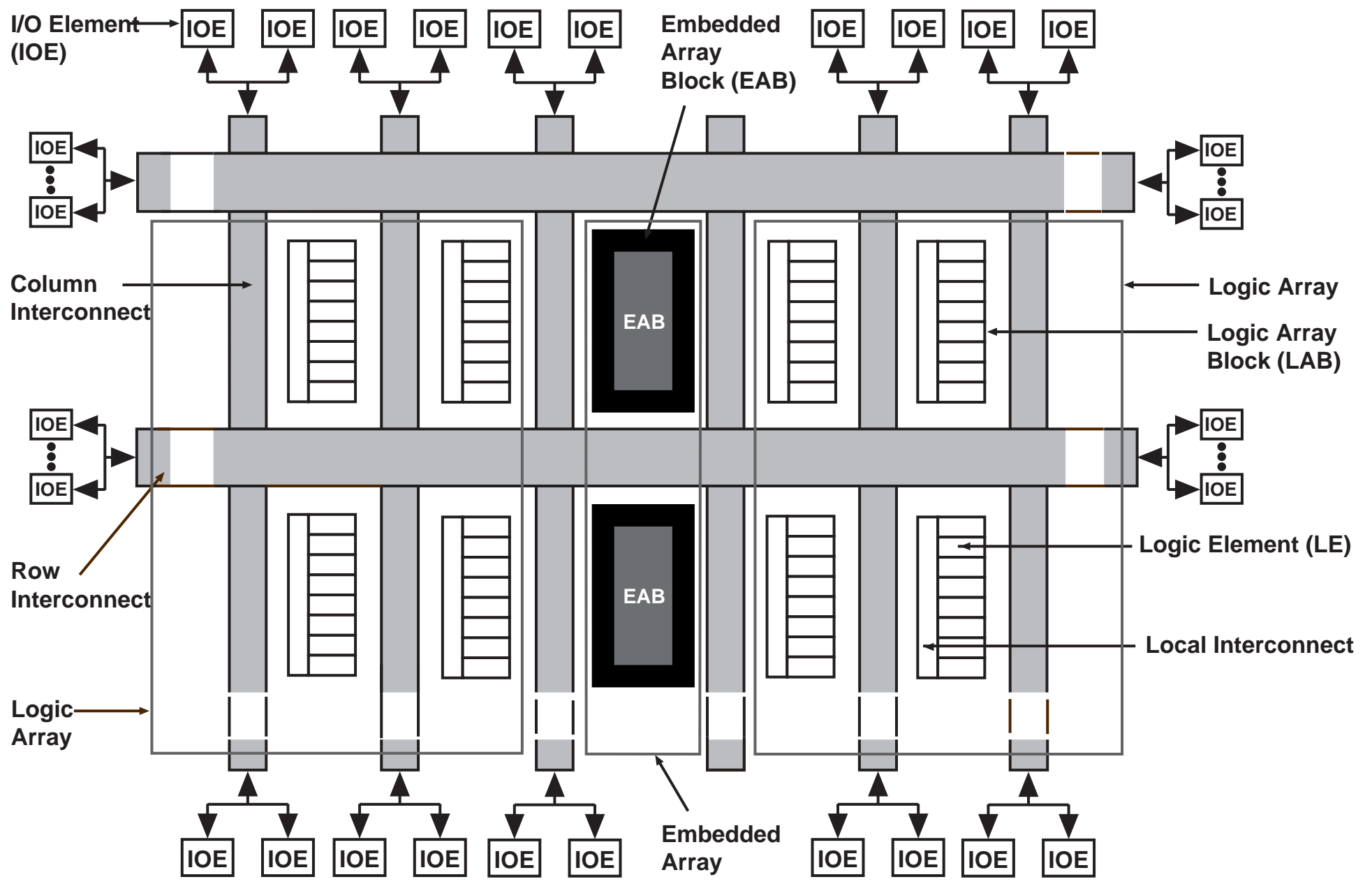


Figure 6-35 FLEX 10K Logic Array Block

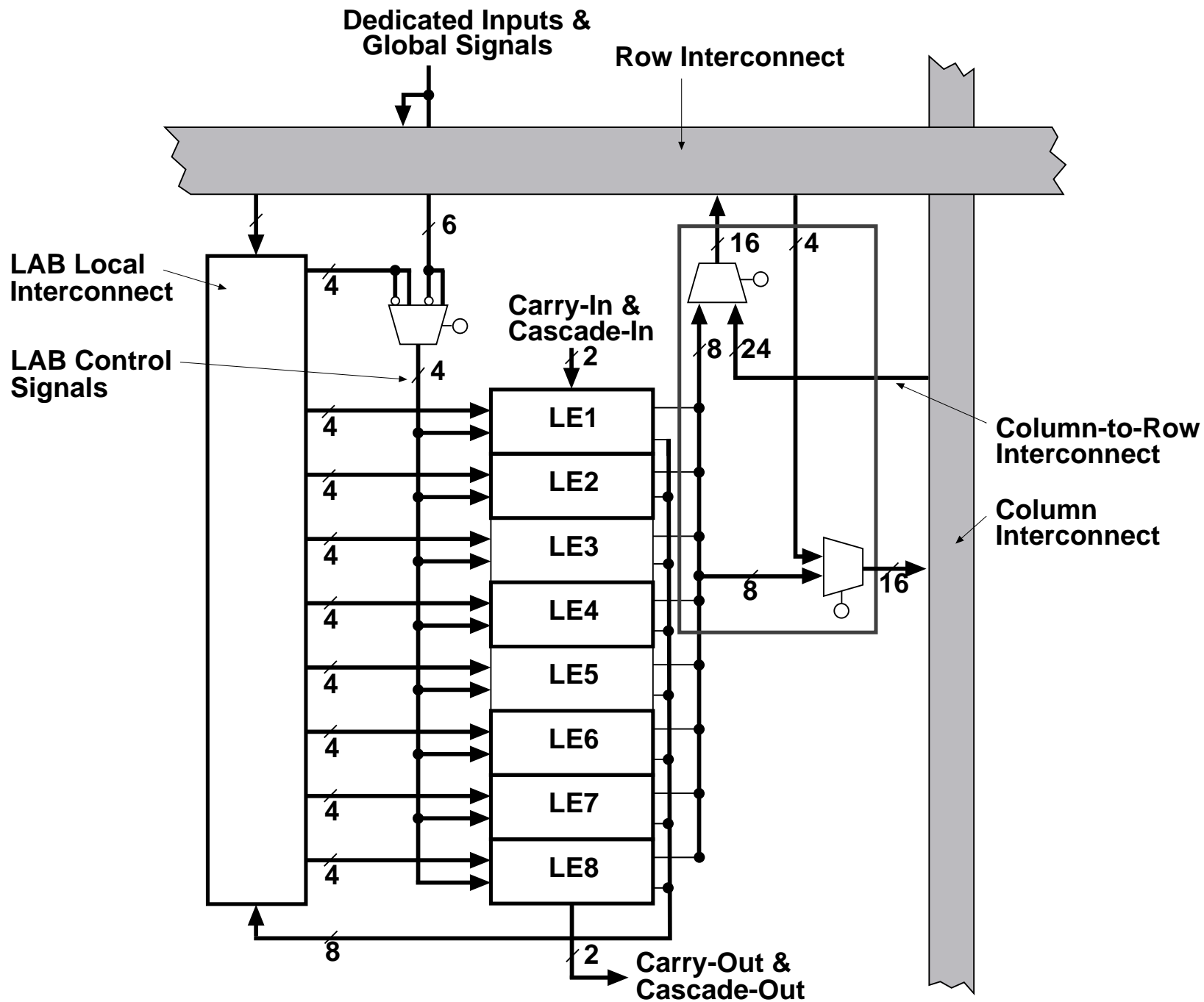


Figure 6-36 FLEX 10K Logic Element


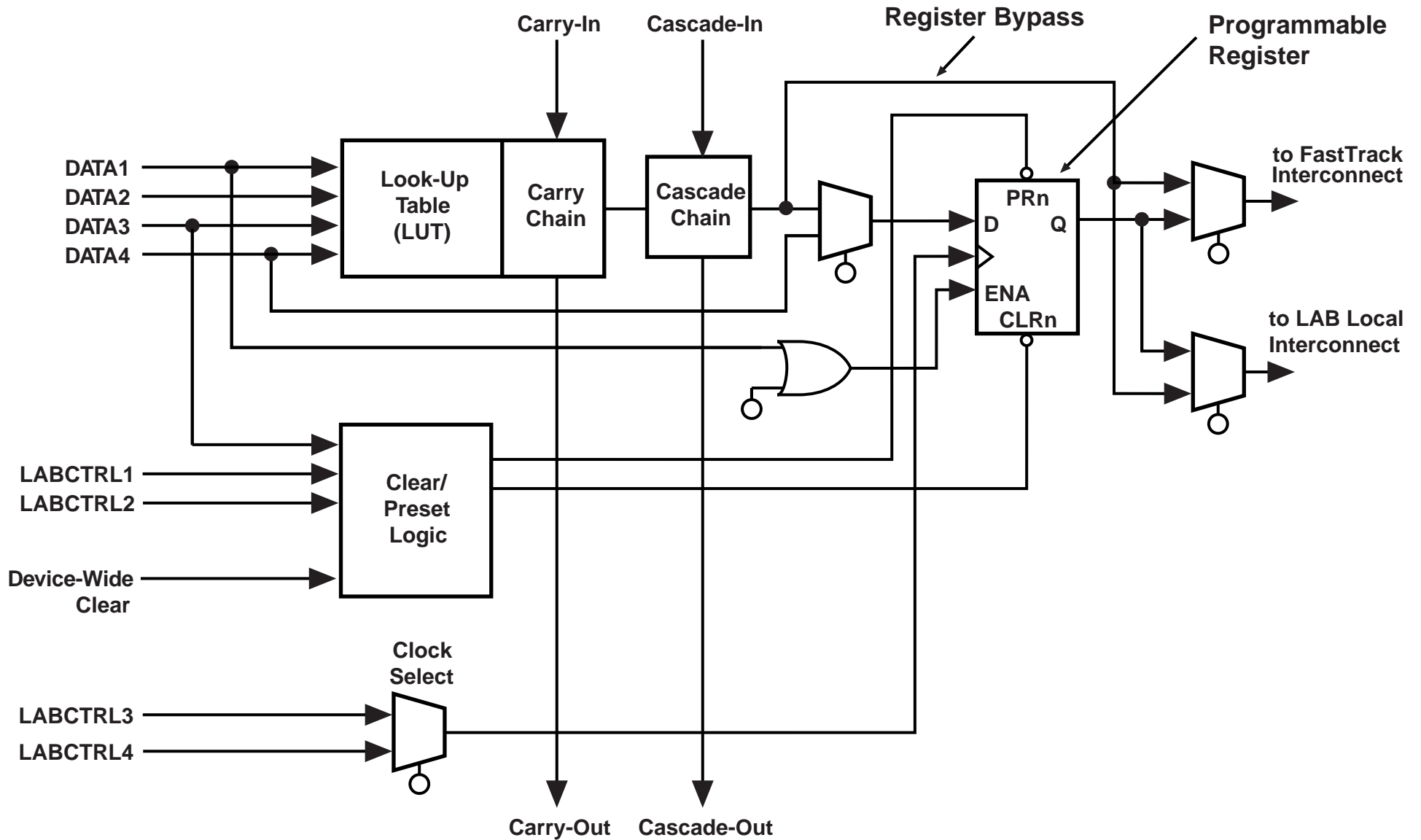


Figure 6-37 Cascade Chain Operation

AND Cascade Chain

 

OR Cascade Chain

 


Figure 6-38 FLEX 10K Embedded Array Block

