

# SIS – Logic Synthesis System

*Luigi Di Guglielmo  
Davide Bresolin  
Tiziano Villa*

University of  
Verona  
Dep. Computer  
Science  
Italy



# Introduction

- *Logic Synthesis* performs the translation from a RTL description (e.g., VHDL) into a design implementation in terms of logic gates, and optimizes the latter
  - It may be driven by different cost functions
    - Area
    - Delay, clock speed
    - etc.
  - It leads to implementations meeting the desired objectives


# *SIS* – Logic Synthesis System (I)

- *SIS* is an interactive tool for synthesis and optimization of sequential circuits
  - developed by the CAD group of U.C. Berkeley in the 1990s
- It produces an optimized net-list preserving the sequential input/output behavior
- It incorporates a set of logic optimization algorithms
  - users can choose among a variety of techniques at each stage of the synthesis process

# *S/S* – Logic Synthesis System (II)

- Different algorithms for various stages of sequential synthesis:
  - State minimization
  - State assignment
  - Node simplification
  - Kernel and cube extraction
  - Technology mapping
  - Retiming

# How to use SIS

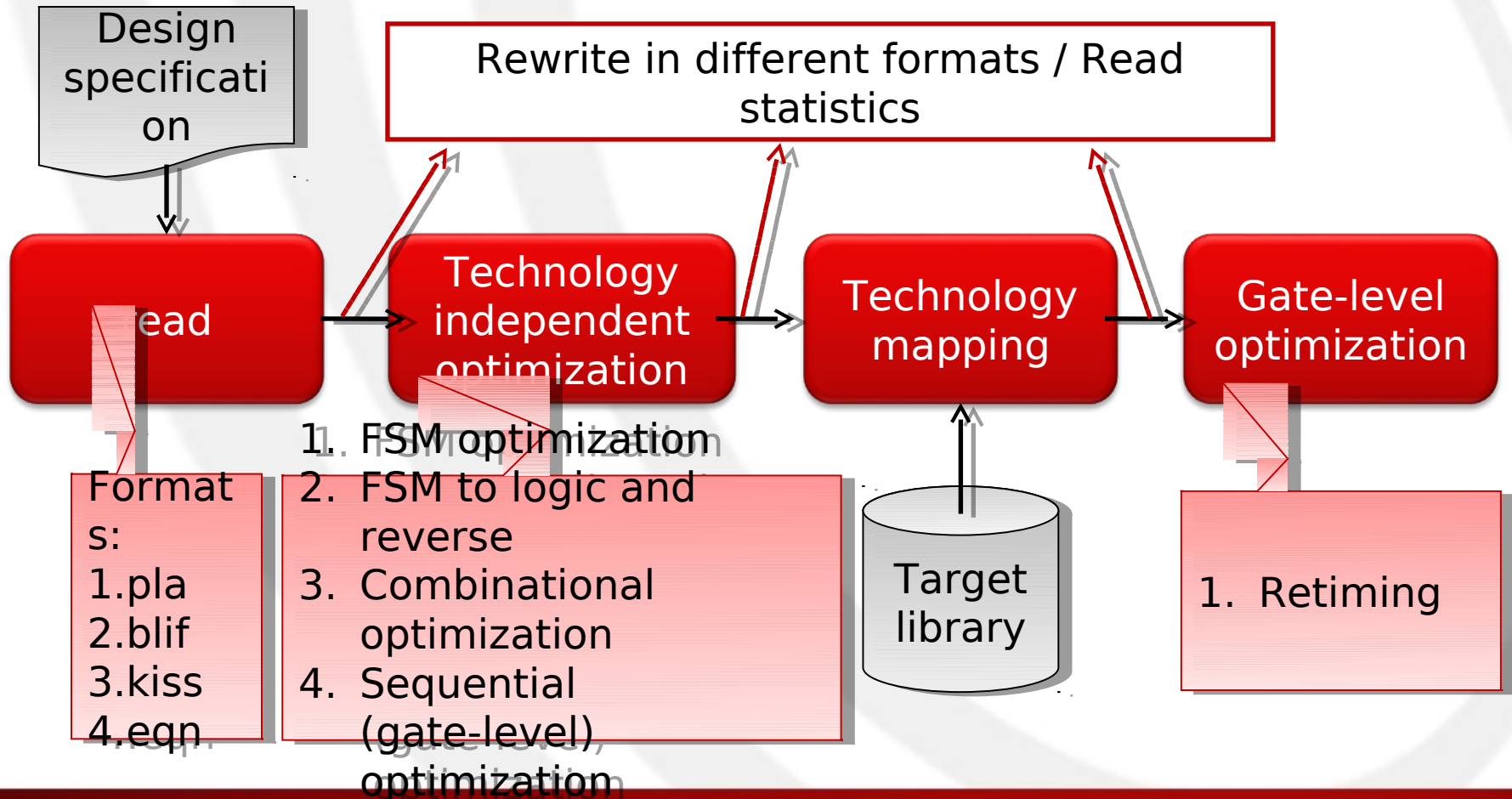

# Design Specification

- A sequential circuit can be input to *SIS* in several ways allowing *SIS* to be used at various stages of the design process
- The most common entry points are
  - Net-list of gates
  - Truth table in PLA (espresso) format
  - Set of equations

- Finite-state machine in state transition table form

# Logic Implementation (Net-list)

- The net-list description is given in extended *BLIF* (Berkeley Logic Interchange Format)
- It consists of interconnected single-output combinational gates and latches
  - Gates are simple elements that perform logical operations
  - Latches store the state

# The SIS Synthesis and Optimization System - Read the specifications

- `$> sis`  
UC Berkeley, SIS 1.3.6 (compiled 2010-11-14 12:35:42)  
`sis>`
- `sis> help`
  - returns a list of all the commands provided by SIS
- `sis> read_pla <file_name>`
  - Loads a pla description
- `sis> read_blif <file_name>`
  - Loads a net-list description
- `sis> read_eqn <file_name>`
  - Loads an equation-based description
- `sis> read_kiss <file_name>`
  - Loads a kiss-style STG description



# The SIS Synthesis and Optimization System - Write the specifications

- `sis> write_pla [file_name]`
  - Writes a PLA description
- `sis> write_blif [file_name]`
  - Writes a net-list description
- `sis> write_eqn [file_name]`
  - Writes an equation-based description
- `sis> write_kiss [file_name]`
  - Writes a kiss-style STG description

# Example 1: the full-adder

```
# full-adder circuit
.i 3
.o 2
.ilb x y z
.ob C S
000 00
001 01
010 01
011 10
100 01
101 10
110 10
111 11
.end
```

- Create a .pla file with the description
- Open the file in SIS
- Try the following commands:
  - print
  - print\_stats
  - print\_io

# The SIS Synthesis and Optimization System - Node simplification (II)

- In *SIS*, the user may invoke the *ESPRESSO* program to perform node simplification
- *sis* > *full\_simplify*
  - the input is a net-list (blif or PLA format)
  - returns a minimized net-list (blif format)
    - *SIS* decomposes multiple output functions into single output functions and represents them separately

# The SIS Synthesis and Optimization System - Node Restructuring

- A logical network can be modified by
  - Creating new nodes
  - Deleting nodes
  - Creating new connections
  - Deleting connections
- A particular case of node restructuring is node creation by extracting a factor from one or more nodes

# The SIS Synthesis and Optimization System – Kernel

(I)

- The extraction of new nodes that are factors of existing nodes is a form of division that may be performed in the Boolean or algebraic domain
- Algebraic techniques: sum-of-products are treated as standard polynomials
  - look for expressions that are observed many times in the nodes of the network and extract such common expressions
  - The extracted expression is implemented only once and the output of that node replaces the expression in any other node
- Current algebraic techniques used in SIS are based on cube-free divisors called *kernels*

# The SIS Synthesis and Optimization System - Kernel (II)

- An expression  $f$  is cube-free if no cubes divides the expression evenly
  - $ab + c$  is cube free
  - $ab+ac$  or  $abc$  are not cube free
- The primary divisors of an expression are obtained by dividing the expression by cubes
- The kernels of an expression are the cube-free primary divisors of the

# The SIS Synthesis and Optimization System - Kernel (III)

- $adf + aef + bdf + bef + cdf + cef + g = (a + b + c)(d + e)f + g$

Kernel	Cokernel
$a + b + c$	$df, ef$
$d + e$	$af, bf, cf$
$(a + b + c)(d + e)$	$f$
$(a + b + c)(d + e)f + g$	$1$

# The SIS Synthesis and Optimization System – Kernel (IV)

- In *SIS*, the user may invoke the command *fast\_extract*, i.e., *fx*, to perform kerneling
- `sis> fx`
  - the input is a net-list
  - extracts common expressions among the nodes and rewrites the nodes of the network in terms of common expressions



# The SIS Synthesis and Optimization System - Technology mapping (I)

- A tree-covering algorithm is used to map arbitrary complex logic gates into cells available in a technology library
- Technology mapping consists of two phases:
  - Decomposing the logic to be mapped into a network of 2-input NAND gates and inverters
  - Covering the network by patterns that represent the possible cells in the library
    - During the covering stage the area or the delay of the circuit is used as an optimization criterion

# The SIS Synthesis and Optimization System - Technology mapping (II)

- In *SIS*, the user may invoke the command *rlib* and *map* to select a library for the technology mapping and perform the mapping, respectively
- `sis> rlib <library_name>`  
`sis> map`
  - the input is a net-list (blif format)
  - map complex logic gates into cells of the chosen technology library (genlib format)

# Mapping the full adder

- Load the *minimal.genlib* library
- Map the full-adder to the library
- Try the following commands:
  - print
  - print\_gate
  - print\_map\_stats

# Example 2: the ticket machine

- Print a ticket after 1.50 euros are deposited
- Single slot for 1 euro and 50 cents coins
- No change



# State Transition Graph (STG) (I)


- A state transition table for a finite-state machine is specified using the KISS format
- It is used in state assignment and state minimization programs
- STG
  - States are symbolic
  - The transition table indicates the next symbolic state and output bit-vector given a current state and an input bit-vector
  - Don't care conditions are indicated by a missing transition or by a '-' in an output bit
    - A present-state/input combination has no explicit next-state/output, or
    - For a present-state/input combination a '-' output stands for either 0 or 1

# State Transition Graph (STG) (II)

```

.start_kiss
.i 2
.o 1
.r q0
00 q0 q0 0
10 q0 q1 0
01 q0 q2 0
00 q1 q1 0
10 q1 q3 0
01 q1 q0 1
00 q2 q2 0
10 q2 q0 1
01 q2 q0 1
00 q3 q3 0
10 q3 q0 1
01 q3 q0 1
.end_kiss
.end

```

 

# The SIS Synthesis and Optimization System - State minimization (I)

- State minimization works on STGs
  - Degrees of freedom (i.e., unspecified transitions or explicit output don't cares) can be exploited to produce a machine with fewer states
- State minimization looks for equivalent states in order to minimize the total number of states
  - Two states are equivalent if they produce the same output sequences given the same input sequences

# The SIS Synthesis and Optimization System - State minimization (II)

- In *SIS*, the user may invoke the *STAMINA* program to perform state minimization
  - *STAMINA* is a state minimizer for incompletely specified machine
- `sis> state_minimize stamina`
  - the input is a STG (kiss format)
  - the original STG is replaced by the one computed by *STAMINA* with (possibly)



# Minimize the Ticket counter FSM

- Create a .kiss2 file with the description of the FSM
- Open the file in SIS
- Minimize the FSM
- Compare the minimized machine with the original one
  - use `write_kiss` to print the minimized FSM

# The SIS Synthesis and Optimization System - State assignment (I)

- State assignment provides the mapping from a STG to a net-list
- State assignment requires a state transition table and computes binary codes for each symbolic state
- Binary codes are used to create a logic level implementation
  - substituting the binary codes for the symbolic states, it creates a latch for each bit of the binary code

# The SIS Synthesis and Optimization System - State assignment (II)

- In *SIS*, the user may invoke either *JEDI* or *NOVA* programs to perform state assignments
- `sis> state_assign nova`  
or  
`sis> state_assign jedi`
  - the input is a STG (kiss format)
  - returns a state assignment of the STG and a corresponding logic implementation (net-list) (blif format)

# State-assign the Ticket counter FSM

- Do the state assignment of the minimized FSM
  - Use *print*, *print\_stats*, and *print\_latch* to obtain information
- Simulate the FSM
  - Use *simulate input1 input2* to give inputs
  - *print\_state* gives the current state of the FSM

# Mapping the ticket counter

- Load the *lib2.genlib* and the *lib2\_latch.genlib* libraries
  - Use *rlib -a* to load the second library!
- Map the ticket counter FSM
- Try the following commands:
  - *print\_stats*
  - *print\_gate*
  - *print\_map\_stats*

# The SIS Synthesis and Optimization System - Retiming (I)

- Retiming is an algorithm that moves registers across logic gates to minimize
  - Cycle time, or
  - Number of registers, or
  - Number of registers subject to a cycle-time constraint
- It operates on synchronous edge-triggered designs
- The sequential I/O behavior of the circuit is maintained

# The SIS Synthesis and Optimization System - Retiming (II)

- In *SIS*, the user may invoke the command *retime* to perform the retiming of the circuit
- `sis> retime`
  - the input is a net-list (blif format)
  - Add more latches, or re-position the latches, to reduce the clock period
    - Generally used to reduce the cycle time of the circuit by adding latches

# Retiming the ticket counter

- Use the command *retime* to optimize the circuit
- Try the following commands:
  - `print_stats`
  - `print_gate`
  - `print_map_stats`
- Simulate the new circuit



# Synthesis and optimizations

- SIS provides scripts for performing logic network optimizations
  - The standard *script*
  - The standard *script.rugged*
  - The standard *script.delay*
- Such scripts derive from the experience of SIS developers

# References – U.C. Berkeley

- More *SIS* infos are available at <http://embedded.eecs.berkeley.edu/pubs/downloads/sis/index.htm>
  - Documentation
  - Examples

