 


## Process “style 4”

- Processes with a sensitivity list including a clock signal, and eventually an asynchronous reset signal. An if statement constitutes the process, sensitive to the clock (and reset) events.

```
Process (ck_name [, reset_name])
begin
    [if (reset_name = value) then
        ... reset behavior
    elsif (ck_name = value and ck_name'event) then
        ... clocked behavior
    end if;
end process;
```


60



## Specifying FSMs

- Selection of:
  - Moore or Mealy style
  - Reset or not
  - Synchronous/asynchronous reset
  - Buffers position
- *Data type definition for State elements*


61

 

## FSMs in VHDL - Examples


- Two problems:
  - Coin handler for can disposal
    - Accepts coins of 50, 100, Selection button
    - When at 150 allows selection and no change
    - When at 200 allows selection and change
  - Bit sequence recognizer
    - Recognizes concatenated sequences
      - ...0110...
      - ...1110...
    - When recognized, output at 1.

62

 


## FSMs in VHDL - Coin Handler - 1

### ➤ Coin handler

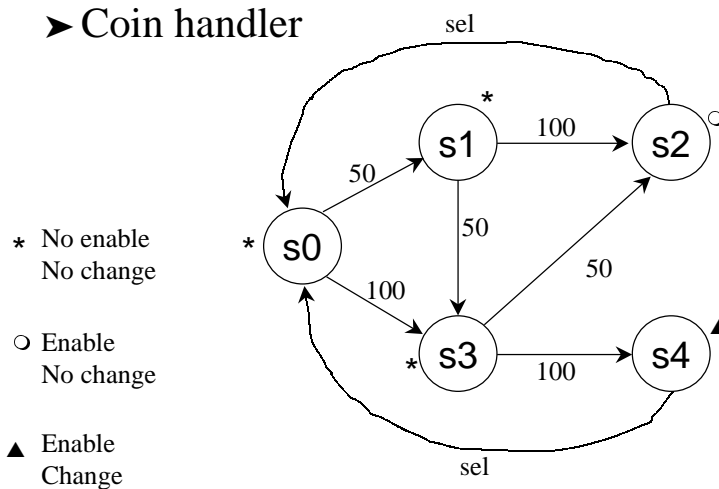

63

 


## FSMs in VHDL - Coin Handler - 2

```
PACKAGE CH_pack IS
    type CHstate is (s0, s1, s2, s3, s4)
END CH_pack;

ENTITY CoinHandler is
    PORT(clk, res: in bit;
         Pin: in bit_vector(1 downto 0);
         --01: 50, 10: 100, 11: sel
         Enab, Change: out bit)
END CoinHandler;
```

64

 


## FSMs in VHDL - Coin Handler - 3

```
ARCHITECTURE fsm OF CoinHandler IS
    signal pstate: CHstate := s0;
    signal nstate: CHstate := s0;
BEGIN
    StateEvol: process(clk, res)
    BEGIN
        IF (clk'EVENT and clk = '1') THEN
            IF (res = '0') THEN
                pstate <= s0;
            ELSE
                pstate <= nstate;
            END IF;
        END IF;
    END PROCESS StateEvol;
```

Synchronous reset signal

Reset active low


65

 

## FSMs in VHDL - Coin Handler - 4

```
NSL: process(pstate, Pin)
BEGIN
  CASE pstate IS
    WHEN 's0' => IF Pin = "01" THEN
      nstate <= s1;
    ELSIF Pin = "10" THEN
      nstate <= s3;
    ELSE
      nstate <= pstate;
    END IF;
    WHEN 's1' => IF Pin = "01" THEN
      nstate <= s2;
    ...
```


66

 

## FSMs in VHDL - Coin Handler - 5

```
    WHEN 's4' => IF Pin = "11" THEN
      nstate <= s0;
    ELSE
      nstate <= pstate;
    END IF;
    WHEN OTHERS => nstate <= s0;
  END CASE;
END PROCESS NSL;
```


67

 


## FSMs in VHDL - Coin Handler - 6

```
OL: Process(pstate)
BEGIN
  CASE pstate IS
    WHEN s0|s1|s3 => Enab = '0';
                     Change = '0';
    WHEN s2 => Enab = '1';
               Change = '0';
    WHEN s4 => Enab = '1';
               Change = '1';
    WHEN OTHERS => Enab = '0';
                  Change = '0';
  END CASE;
END Process OL;
END fsm;
```


68

 

## FSMs in VHDL - Recognizer - 1

 


69

 

 
## FSMs in VHDL - Recognizer - 2

```
PACKAGE RecognPack IS
    type Rstate is (a, b, c, d);
END RecognPack;

ENTITY Recognizer is
    PORT(clk: in bit;
         PI: in bit;
         Z: out bit)
END Recognizer ;
```




70

 

## FSMs in VHDL - Recognizer - 3

```
ARCHITECTURE ThreeProc OF Recognizer IS
    signal pstate, nstate: Rstate := a;
BEGIN
    NextState: PROCESS
    BEGIN
        WAIT UNTIL clk = '1' AND clk'EVENT
        CASE pstate IS
            WHEN a => IF PI = '1' THEN
                        nstate <= b;
                    ELSE
                        nstate <= a;
                    END IF;
            WHEN b => IF PI = '1' THEN
                        nstate <= c;
                    ELSE
                        nstate <= a;
                    END IF;
        END CASE;
    END PROCESS;
END ThreeProc;
```


71

 

## FSMs in VHDL - Recognizer - 4

```
    WHEN c => IF PI = '1' THEN
        nstate <= d;
    ELSE
        nstate <= a;
    END IF;
    WHEN d => IF PI = '1' THEN
        nstate <= c;
    ELSE
        nstate <= a;
    END IF;
    WHEN OTHERS => nstate <= a;
END CASE;
END PROCESS NextState;
```

72

 

## FSMs in VHDL - Recognizer - 5

```
Output: PROCESS(pstate, PI)
BEGIN
    CASE pstate IS
        WHEN a => Z <= '0';
        WHEN b => Z <= '0';
        WHEN c => IF PI = '1' THEN
            Z <= '0';
        ELSE
            Z <= '1';
        END IF;
        WHEN d => IF PI = '1' THEN
            Z <= '0';
        ELSE
            Z <= '1';
        END IF;
        WHEN OTHERS => Z <= '0';
    END CASE;
END PROCESS;
```


73

## FSMs in VHDL - Recognizer - 6

```
StateEvol: Process
begin
    WAIT UNTIL clk'EVENT and clk = '1';
    pstate <= nstate;
end process;
end ThreeProc;
```

74

## FSMs in VHDL - Recognizer - 7

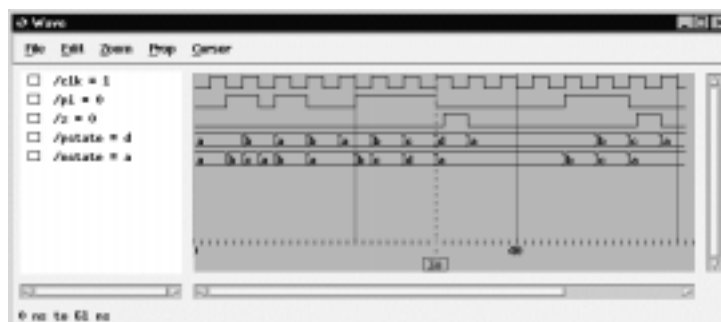

75




## FSMs in VHDL - Recognizer - 8



## FSMs in VHDL - Recognizer - 9




 

## Sequential elements - summary

- Latch inference
  - No specified assignment for a conditional branch
  - It is not possible to model latches using variables
- Clock inference
  - CLK = '1' AND clk'EVENT
  - type: Bit, Boolean, Std\_ulogic, Std\_logic
  - No ELSE clause in the IF statement checking the clock edge


78

 

## Signals: wires or memory?

- Latches are inferred when signals are not assigned in all conditional branch.
- Latches are inferred each time an assignment is made before a wait until statement
- Memory (not latches) is inferred on variables anytime it is necessary to store data for subsequent simulation steps.

79

 

## Synthesis guidelines

- Data Flow statements translate into combinational logic
- Sequential logic is specified in a **PROCESS** statement that includes a Clock signal.
- Explicit State Machines contain one **WAIT UNTIL CLOCK'EDGE** in a process, with a **CASE** statement describing the FSM.
- Implicit State Machines contain multiple **WAIT UNTIL CLOCK'EDGE** in a process without a sensitivity list.